



Dr. H N National College of Engineering  
Approved by All India Council for Technical Education  
(AICTE), Govt. of India and affiliated to Visvesvaraya  
Technological University (VTU)  
36B Cross, Jayanagar 7th block, Bengaluru – 560070



## **DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING**

### **Course: Digital Design and Computer Organization**

**Course Code: BCS302**  
**III-SEMESTER**

**[AS PER OUTCOME BASED EDUCATION (OBE) AND CHOICE BASED CREDIT  
SYSTEM (CBCS) 2025 SCHEME]**

**Academic Year – 2025-2026**

**LAB MANUAL**

**Prepared by:**

**Dr. Purushottam U & Mr. Sunil Kumar S**  
**Department of CSE**

### **Our Vision**

To impart perseverant education leading to greater heights

### **Our Mission**

- By providing well-designed physical infrastructure with technology with a supportive community
- By building resilience through self-awareness, stress management and growth mind set
- By developing a sense of responsibility and accountability
- By developing empathy, integrity, self-reflection and self-improvement

**VISVESVARAYA TECHNOLOGICAL UNIVERSITY, BELAGAVI**

**B.E. in Computer Science and Engineering**

**Scheme of Teaching and Examinations 2022**

**Outcome-Based Education (OBE) and Choice Based Credit System (CBCS)**

**(Effective from the academic year 2025 - 26)**

**Integrated Professional Core Course (IPCC)**

Refers to Professional Theory Core Course Integrated with Practical is of the same course

**Course: Digital Design and Computer Organization**

**Course Code: BCS302**

## TABLE OF CONTENTS

Item
<b>Program Outcomes (POs) and Program Specific Outcomes (PSOs)</b>
<b>Syllabus-</b> Course Objectives & Suggested Learning Resources
<b>Course Outcomes-</b> Mapping of Course Outcomes with POs & PSOs
<b>Assessment Details (both CIE and SEE) -Scheme of Evaluation</b>
<b>List of Major Equipment</b>
<b>List of Experiment/Programs &amp; Additional Experiment/Programs</b>

**PROGRAM EDUCATIONAL OBJECTIVES (PEOs)**

After 4 years of graduation, graduates will be able to

**PEO1:** To develop in students, the ability to solve real life problems by applying fundamental science and elementary strengths of computer science courses.

**PEO2:** To mould students, to have a successful career in the IT industry where graduates will be able to design and implement the needs of society and nation.

**PEO3:** To transform students, to excel in a competitive world through higher education and indulge in research through continuous learning process.

## **PROGRAM OUTCOMES (POs)**

- PO1: Engineering Knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- PO2: Problem Analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- PO3: Design/Development of Solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- PO4: Conduct Investigations of Complex Problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
- PO5: Modern Tool Usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modelling to complex engineering activities with an understanding of the limitations.
- PO6: The Engineer and Society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- PO7: Environment and Sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- PO8: Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
- PO9: Individual and Team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
- PO10: Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
- PO11: Project Management and Finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
- PO12: Life-Long Learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

## **PROGRAM SPECIFIC OUTCOMES (PSOs)**

At the end of the program, graduates will be able to

- PSO1:** Apply engineering principles, professional ethics and fundamental science in designing systems and communication models (protocols).
- PSO2:** Design and develop smart and intelligent based applications in computational environment.

## SYLLABUS

**DIGITAL CIRCUIT AND COMPUTER ORGANIZATION LABORATORY**

[As per Choice Based Credit System (CBCS) scheme]

(Effective from the academic year 2022 -2023)

**SEMESTER – III**

Course Code	<b>BCS302</b>	CIE Marks	50
Teaching Hours/Week (L:T:P: S)	3:0:2:0	SEE Marks	50
Total Hours of Pedagogy	40 hours Theory + 20 Hours of Practicals	Total Marks	100
Credits	<b>04</b>	Exam Hours	03

**Course Learning Objectives:**

CLO 1: To demonstrate the functionalities of binary logic system.

CLO 2: To explain the working of combinational and sequential logic system.

CLO 3: To realize the basic structure of computer system.

CLO 4: To illustrate the working of I/O operations and processing unit.

**Teaching-Learning Process (General Instructions)**

These are sample Strategies; that teachers can use to accelerate the attainment of the various course outcomes.

1. Chalk and Talk
2. Live Demo with experiments
3. Power point presentation

**Module-1**

**Introduction to Digital Design:** Binary Logic, Basic Theorems And Properties Of Boolean Algebra, Boolean Functions, Digital Logic Gates, Introduction, The Map Method, Four-Variable Map, Don't-Care Conditions, NAND and NOR Implementation, Other Hardware Description Language – Verilog Model of a simple circuit.

**Text book 1: 1.9, 2.4, 2.5, 2.8, 3.1, 3.2, 3.3, 3.5, 3.6, 3.9****Module-2**

**Combinational Logic:** Introduction, Combinational Circuits, Design Procedure, Binary Adder - Subtractor, Decoders, Encoders, Multiplexers. HDL Models of Combinational Circuits – Adder, Multiplexer, Encoder. **Sequential Logic:** Introduction, Sequential Circuits, Storage Elements: Latches, Flip-Flops.

**Text book 1: 4.1, 4.2, 4.4, 4.5, 4.9, 4.10, 4.11, 4.12, 5.1, 5.2, 5.3, 5.4****Module-3**

**Basic Structure of Computers:** Functional Units, Basic Operational Concepts, Bus structure, Performance – Processor Clock, Basic Performance Equation, Clock Rate, Performance Measurement. **Machine Instructions and Programs:** Memory Location and Addresses, Memory Operations, Instruction and Instruction sequencing, Addressing Modes.

**Text book 2: 1.2, 1.3, 1.4, 1.6, 2.2, 2.3, 2.4, 2.5****Module-4**

**Input/output Organization:** Accessing I/O Devices, Interrupts – Interrupt Hardware, Enabling and Disabling Interrupts, Handling Multiple Devices,

**Direct Memory Access:** Bus Arbitration, Speed, size and Cost of memory systems. Cache Memories – Mapping Functions.

**Text book 2: 4.1, 4.2.1, 4.2.2, 4.2.3, 4.4, 5.4, 5.5.1**

Module-5	
<b>Basic Processing Unit:</b> Some Fundamental Concepts: Register Transfers, Performing ALU operations, fetching a word from Memory, Storing a word in memory. Execution of a Complete Instruction. <b>Pipelining:</b> Basic concepts, Role of Cache memory, Pipeline Performance. <b>Text book 2: 7.1, 7.2, 8.1</b>	
PRACTICAL COMPONENT OF IPCC	
Sl. No	Experiments Simulation packages preferred: Multisim, Modelsim, PSpice or any other relevant
1	Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates.
2	Design a 4 bit full adder and subtractor and simulate the same using basic gates.
3	Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.
4	Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.
5	Design Verilog HDL to implement Decimal adder.
6	Design Verilog program to implement Different types of multiplexer like 2:1, 4:1 and 8:1.
7	Design Verilog program to implement types of De-Multiplexer.
8	Design Verilog program for implementing various types of Flip-Flops such as SR, JK and D.
<b>Course outcome (Course Skill Set)</b> At the end of the course, the student will be able to: <b>CO1: Apply</b> the K–Map techniques to simplify various Boolean expressions. <b>CO2: Design</b> different types of combinational and sequential circuits along with Verilog programs. <b>CO3: Describe</b> the fundamentals of machine instructions, addressing modes and Processor performance. <b>CO4: Explain</b> the approaches involved in achieving communication between processor and I/O devices. <b>CO5: Analyze</b> internal Organization of Memory and Impact of cache/Pipelining on Processor Performance.	
<b>Suggested Learning Resources:</b>  <b>Textbooks</b> 1. M. Morris Mano & Michael D. Ciletti, Digital Design With an Introduction to Verilog Design, 5e, Pearson Education. 2. Carl Hamacher, Zvonko Vranesic, Safwat Zaky, Computer Organization, 5th Edition, Tata McGraw Hill.	
<b>Weblinks and Video Lectures (e-Resources):</b> <a href="https://cse11-iiith.vlabs.ac.in/">https://cse11-iiith.vlabs.ac.in/</a>	
<b>Activity Based Learning (Suggested Activities in Class)/ Practical Based learning</b> Assign the group task to Design the various types of counters and display the output accordingly <b>Assessment Methods</b> <ul style="list-style-type: none"> <li>• Lab Assessment (25 Marks)</li> <li>• GATE Based Aptitude Test</li> </ul>	

## COURSE OUTCOMES

**At the end of the course the student will be able to:**

**CO1:** Apply the K–Map techniques to simplify various Boolean expressions.

**CO2:** Design different types of combinational and sequential circuits along with Verilog programs.

**CO3:** Describe the fundamentals of machine instructions, addressing modes and Processor performance.

**CO4:** Explain the approaches involved in achieving communication between processor and I/O devices.

**CO5:** Analyze internal Organization of Memory and Impact of cache/Pipelining on Processor Performance.

### Mapping of Course Outcomes with POs & PSOs

Course Outcomes (COs)	Program Outcomes (POs)												Program Specific Outcomes (PSOs)	
	1	2	3	4	5	6	7	8	9	10	11	12	1	2
<b>CO1</b>	2	2	-	-	3	-	-	-	1	1	-	-	1	-
<b>CO2</b>	2	2	2	2	3	-	-	-	1	1	-	-	1	-
<b>CO3</b>	2	2	-	-	-	-	-	-	-	-	-	-	1	-
<b>CO4</b>	2	2	-	-	-	-	-	-	-	-	-	-	-	1
<b>CO5</b>	2	2	2	-	-	-	-	-	-	-	-	-	-	1
<b>Average</b>	<b>2</b>	<b>2</b>	<b>2</b>	<b>2</b>	<b>3</b>	-	-	-	<b>1</b>	<b>1</b>	-	-	<b>1</b>	<b>1</b>



## ASSESSMENT DETAILS (BOTH CIE AND SEE)

- The weightage of Continuous Internal Evaluation (CIE) is 50% and for Semester End Exam (SEE) is 50%. The minimum passing mark for the CIE is 40% of the maximum marks (20 marks out of 50) and for the SEE minimum passing mark is 35% of the maximum marks (18 out of 50 marks).
- A student shall be deemed to have satisfied the academic requirements and earned the credits allotted to each subject/ course if the student secures a minimum of 40% (40 marks out of 100) in the sum of the CIE (Continuous Internal Evaluation) and SEE (Semester End Examination) taken together.
- IPCC means practical portion integrated with the theory of the course.
- CIE marks for the theory component are **25 marks** and that for the practical component is **25 marks**.

### CONTINUOUS INTERNAL EVALUATION (CIE) for IPCC:

CIE THEORY + CIE PRACTICAL

#### ❖ CIE for the theory component of the IPCC (Maximum Marks 25)

- **25 marks for the theory component** are split into
  - **15 marks** for two Internal Assessment Tests (Average of Two Tests each of 25 Marks , scale down the marks scored to 15 marks)
    - The first test at the end of 40-50% coverage of the syllabus and
    - The second test after covering 85-90% of the syllabus
  - **10 marks** for other assessment methods mentioned in 22OB4.2.
- Scaled-down marks of the sum of two tests and other assessment methods will be CIE marks for the theory component of IPCC (that is for 25 marks).
- The student has to secure 40% of 25 marks (10 marks) to qualify in the CIE of the theory component of IPCC.

#### ❖ CIE for the practical component of the IPCC (Maximum Marks 25)

- **25 marks for the practical component** are split into
  - **15 marks** for the conduction of the experiment and preparation of laboratory record, and **10 marks** for the test to be conducted after the completion of all the laboratory sessions.
  - On completion of every experiment/program in the laboratory, the students shall be evaluated including viva-voce and marks shall be awarded on the same day.

- The CIE marks awarded in the case of the Practical component shall be based on the continuous evaluation of the laboratory report. Each experiment report can be evaluated for 10 marks. Marks of all experiments' write-ups are added and scaled down to **15 marks**.
- The laboratory test (duration 02/03 hours) after completion of all the experiments shall be conducted for **50 marks** and scaled down to **10 marks**.
- Scaled-down marks of write-up evaluations and tests added will be CIE marks for the laboratory component of IPCC for **25 marks**.
- The student has to secure 40% of 25 marks to qualify in the CIE of the practical component of the IPCC.

### Split-up of Marks used Practical Sessions

Rubrics No.	Practical Sessions- Continuation Evaluation (CE) Methodology / Process Steps per Experiment	Marks
#R1	Observation	10
#R2	Record writing: Write up of Procedure / Algorithm/ Program and Execution/conduction of experiment	30
#R3	Viva – Voce (Questions & Answers on relevant Experiment /Topic)	10
<b>Total Marks</b> (Note: Conduction of experiment's and Preparation of Laboratory records etc. for 50 Marks scale down the marks scored to 15 marks)		<b>50</b> <b>(Scale down to 15)</b>
Rubrics No.	Practical Sessions-Internal Assessment (IA)	Marks
#R1	Write-up of Procedure/Program/Algorithm	10
#R2	Conduction/Execution	30
#R3	Viva-Voce	10
<b>Total Marks</b> (Note: One test after all experiment's conduction for 50 Marks scale down the marks scored to 10 marks)		<b>50</b> <b>(Scale down to 10)</b>

### SEMESTER END EXAMINATION (SEE) for IPCC:

Theory SEE will be conducted by University as per the scheduled timetable, with common question papers for the course (**duration 03 hours**)

1. The question paper will have ten questions. Each question is set for 20 marks.
2. There will be 2 questions from each module. Each of the two questions under a module (with a maximum of 3 sub-questions), **should have a mix of topics** under that module.
3. The students have to answer 5 full questions, selecting one full question from each module.
4. Marks scored by the student shall be proportionally scaled down to 50 Marks

The theory portion of the IPCC shall be for both CIE and SEE, whereas the practical portion will have a CIE component only. Questions mentioned in the SEE paper may include questions from the practical component.

To put it simply, evaluation techniques/methods are listed in the table for further understanding

Evaluation Type	Maximum Marks	Minimum Passing Marks	Evaluation Details
CIE-IA Tests	15	06	Average of Two Tests each of 25 Marks, scale down the marks scored to 15 marks
CIE-CCAs	10	04	Any two assignment methods as per clause 22OB4.2 of Regulations (if assessment is project based, then one assessment method may be adopted)
<b>Total CIE Theory</b>	<b>25</b>	<b>10</b>	<b>Scale down marks of tests and assignments to 25</b>
CIE Practical	15	06	Conduction of experiment's and Preparation of Laboratory records etc....
CIE Practical Test	10	04	One test after all experiment's conduction for 50 Marks scale down the marks scored to 10 marks
<b>Total CIE Practical</b>	<b>25</b>	<b>10</b>	<b>Scale down marks of experiment's record and test to 25</b>
<b>TOTAL CIE= Total CIE Theory + Total CIE Practical</b>	<b>50</b>	<b>20</b>	
<b>SEE</b>	<b>50</b>	<b>18</b>	SEE exam is a theory exam, conducted for 100 marks are scaled down to 50 marks
<b>CIE+SEE</b>	<b>100</b>	<b>40</b>	

**LIST OF EXPERIMENT/PROGRAMS**

<b>Expt. No.</b>	<b>Details</b>
	<b>INTRODUCTION</b>
1	Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates.
2	Design a 4 bit full adder and subtractor and simulate the same using basic gates.
3	Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.
4	Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.
5	Design Verilog HDL to implement Decimal adder.
6	Design Verilog program to implement Different types of multiplexer like 2:1, 4:1 and 8:1.
7	Design Verilog program to implement types of De-Multiplexer.
8	Design Verilog program for implementing various types of Flip-Flops such as SR, JK and D.
	VIVA-VOCE
	APPENDIX


## INTRODUCTION

### ❖ Introduction to the Multisim Interface

Multisim is the schematic capture and simulation application of National Instruments Circuit Design Suite, a suite of EDA (Electronics Design Automation) tools that assists you in carrying out the major steps in the circuit design flow. It provides a virtual environment for designing, testing, and simulating electronic circuits. Multisim allows users to create schematic diagrams, simulate circuit behavior, and analyze circuit performance. Multisim is designed for schematic entry, simulation, and feeding to downstage steps, such as PCB layout.
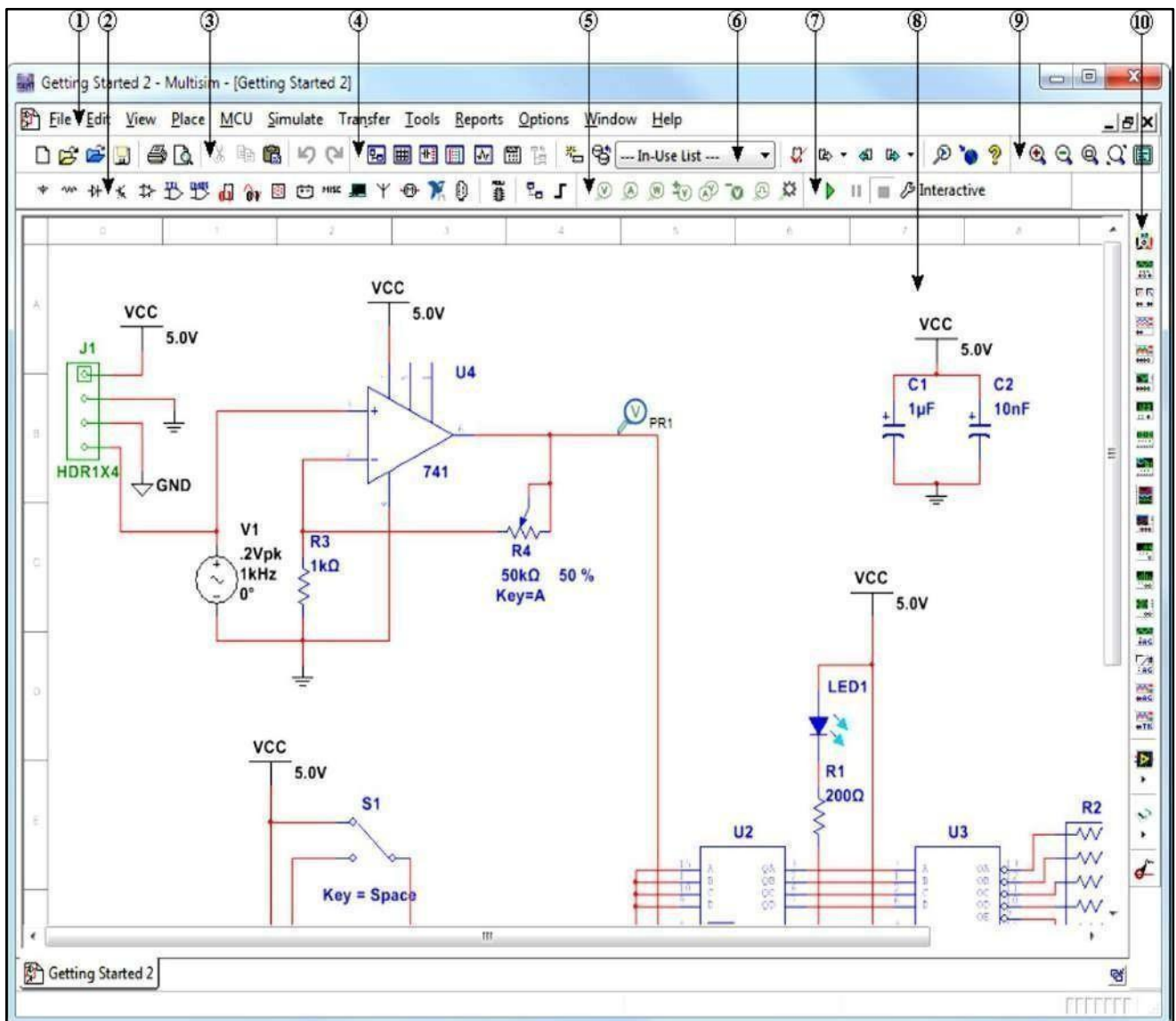
### Multisim User Interface

The Multisim user interface includes the following elements:



Refer to the table below as needed:

	Element	Description
1	Menu Bar	Contains the commands for all functions.
2	Component Toolbar	Contains buttons that you use to select components from the Multisim database for placement in your schematic.
3	Standard Toolbar	Contains buttons for commonly-performed functions such as Save, Print, Cut, and Paste.
4	Main Toolbar	Contains buttons for common Multisim functions.
5	Place Probe Toolbar	Contains buttons that you use to place various types of probes on the design. You can also access <b>Probe Settings</b> from here.
6	In-Use Toolbar	Contains a list of all components used in the design.
7	Simulation Toolbar	Contains buttons for starting, stopping and pausing simulation.
8	Workspace	This is where you build your designs.
9	View Toolbar	Contains buttons for modifying the way the screen is displayed.
10	Instruments Toolbar	Contains buttons for each instrument.








 



**Installation steps are given below:** Install Multisim by obtaining the software from National Instruments and following the provided installation instructions.

1. Launch Multisim and choose to **create a new project** or open an existing one from the start page.
2. Create a **new project** by giving it a name and choosing a save location.
3. Within the project, create a schematic by clicking "**New**" and selecting "**Schematic**."
4. Build your circuit on the schematic canvas by dragging components from the library and connecting them with wiring tools.
5. Optionally, add virtual instruments like oscilloscopes or multimeters to visualize and analyze your circuit during simulation.
6. Simulate your circuit by clicking on the "**Simulate**" tab, choosing the simulation type, adjusting settings, and clicking "**Run**."
7. Analyze simulation results using built-in instruments, graphs, and charts to understand circuit behavior.
8. Optionally, transfer your schematic to NI Ultiboard for PCB layout by clicking "Transfer to Ultiboard."
9. Save your project periodically, export simulation results or other data as needed, and close Multisim when finished.














## Standard Toolbar








The **Standard** toolbar contains buttons for commonly performed functions. Its buttons are described below:

Button	Description
	<b>New</b> button. Creates a new circuit file.
	<b>Open</b> button. Opens an existing circuit file.
	<b>Open Sample</b> button. Opens a folder containing sample and getting started files.
	<b>Save</b> button. Saves the active circuit.
	<b>Print Circuit</b> button. Prints the active circuit.
	<b>Print Preview</b> button. Previews the circuit as it will be printed.
	<b>Cut</b> button. Removes the selected elements and places them on the Windows clipboard.
	<b>Copy</b> button. Copies the selected elements and places them on the Windows clipboard.
	<b>Paste</b> button. Inserts the contents of the Windows clipboard at the cursor location.
	<b>Undo</b> button. Undoes the most recently performed action.
	<b>Redo</b> button. Redoes the most recently performed undo.

## Components Toolbar





The buttons in the Components toolbar are described below. Each button will launch the place component browser (Select a Component browser) with the group specified on the button pre-selected.

Button	Description
	<b>Place Source</b> button. Selects the <b>Source</b> components group in the browser.
	<b>Place Basic</b> button. Selects the <b>Basic</b> components group in the browser.
	<b>Place Diode</b> button. Selects the <b>Diode</b> components group in the browser.
	<b>Place Transistor</b> button. Selects the <b>Transistor</b> components group in the browser.
	<b>Place Analog</b> button. Selects the <b>Analog</b> components group in the browser.
	<b>Place TTL</b> button. Selects the <b>TTL</b> components group in the browser.
	<b>Place CMOS</b> button. Selects the <b>CMOS</b> component group in the browser.
	<b>Place Miscellaneous Digital</b> button. Selects the <b>Miscellaneous Digital</b> component group in the browser.
	<b>Place Mixed</b> button. Selects the <b>Mixed</b> component group in the browser.
	<b>Place Power Components</b> button. Selects the <b>Power</b> component group in the browser.
	<b>Place Indicator</b> button. Selects the <b>Indicator</b> component group in the browser.

Button	Description
	<b>Place Miscellaneous</b> button. Selects the <b>Miscellaneous</b> component group in the browser.
	<b>Place Advanced Peripherals</b> button. Selects the <b>Advanced Peripherals</b> component group in the browser.
	<b>Place RF</b> button. Selects the <b>RF</b> component group in the browser.
	<b>Place Electromechanical</b> button. Selects the <b>Electromechanical</b> component group in the browser.
	<b>Place MCU</b> button. Selects the <b>MCU</b> component group in the browser.
	<b>Place Hierarchical Block</b> button. Opens a file to be embedded as a hierarchical block. Refer to the <i>Hierarchical Design</i> section of Chapter 4, <i>Working with Larger Designs</i> , for more information.
	<b>Place Bus</b> button. Places a bus with segments created as you click on the workspace. Refer to the <i>Buses</i> section of Chapter 4, <i>Working with Larger Designs</i> , for more information.

## Simulation Toolbar

The **Simulation** toolbar contains buttons used during simulation.

Button	Description
	<b>Run/resume simulation</b> button. Starts/resumes simulation of the active circuit. Refer to the <i>Start/Stop/Pause Simulation</i> section of Chapter 8, <i>Simulation</i> , for more information.
	<b>Pause simulation</b> button. Pauses simulation. Refer to the <i>Start/Stop/Pause Simulation</i> section of Chapter 8, <i>Simulation</i> , for more information.
	<b>Stop simulation</b> button. Stops the simulation. Refer to the <i>Start/Stop/Pause Simulation</i> section of Chapter 8, <i>Simulation</i> , for more information.
	<b>Pause at Next MCU Instruction Boundary</b> button. Refer to the <i>Stepping and Breaking</i> section for more information.

## OVERVIEW OF HDL

Hardware Description Languages (HDLs) are specialized programming languages used for the design, modeling, and simulation of digital circuits and systems. HDLs allow engineers to describe the behavior and structure of electronic circuits at various levels of abstraction. Here is an overview of HDLs:

### Purpose of HDLs:

1. **Digital Circuit Design:** HDLs are primarily used for designing digital circuits, including processors, memory units, controllers, and other digital components.
2. **Simulation:** HDLs facilitate the simulation of digital circuits before actual implementation, helping designers to verify functionality and detect potential issues.
3. **Synthesis:** HDLs support synthesis tools that convert high-level hardware descriptions into low-level representations suitable for implementation on programmable devices like FPGAs or ASICs.

### Types of HDLs:

1. **Verilog:** Verilog is one of the most widely used HDLs. It supports both behavioral and structural modeling and is used for simulating and synthesizing digital circuits.
2. **VHDL (VHSIC Hardware Description Language):** VHDL is another popular HDL used for modeling digital circuits. It was developed by the U.S. Department of Defense and is known for its strong type-checking and suitability for complex systems.

### Levels of Abstraction:

1. **Behavioral Modeling:** Describes the functionality of a circuit without specifying its structure. It includes high-level constructs like processes, tasks, and functions.
2. **Structural Modeling:** Describes a circuit in terms of its components and their interconnections.



It uses primitive logic gates, flip-flops, and instances of other modules.

3. **RTL (Register-Transfer Level):** Describes the flow of data between registers. It is often used for synthesis and represents a mid-level abstraction.
4. **Gate-Level Modeling:** Describes the circuit using logic gates and flip-flops. This level is close to the actual hardware implementation.

Applications:

1. **ASIC (Application-Specific Integrated Circuit) Design:** HDLs are commonly used in ASIC design to create custom integrated circuits tailored for specific applications.
2. **FPGA (Field-Programmable Gate Array) Design:** FPGAs can be programmed using HDLs to implement digital circuits on reconfigurable hardware.
3. **Digital Signal Processing:** HDLs are used in the design of digital signal processing circuits for applications such as communication systems and audio processing.

Verilog is a hardware description language (HDL) used for the modeling and design of digital systems. It is widely used in the field of electronic design automation (EDA) for both simulation and synthesis of digital circuits. Here are key aspects of Verilog:

1. **Modules:** Verilog designs are organized into modules, representing logical units of a digital circuit.
2. **Ports:** Modules have input and output ports, which define the signals entering and leaving the module.
3. **Data Types:** Verilog supports various data types including wire for connections, reg for registers, and integer for integers.
4. **Behavioral Modeling:** Describes the functionality of a circuit without specifying its structure using constructs like always blocks.
5. **Structural Modeling:** Describes a circuit in terms of its components and how they are interconnected using gate-level primitives and module instances.
6. **Data Flow Modeling:** Describes how data moves through a circuit based on the relationships between signals using continuous assignment statements.
7. **Procedural Blocks:** Verilog uses procedural blocks like always, initial, and assign for describing the behavior of a circuit at different levels of abstraction.
8. **Sequential Logic:** Supports modeling of flip-flops, latches, and other sequential logic elements for building state machines and memory elements.
9. **Testbenches:** Testbenches are written in Verilog to verify the correctness of a design through simulation.
10. **Simulation:** Verilog is commonly used for simulation using tools like ModelSim or VCS to validate and debug designs before implementation.

**11. Synthesis:** Verilog can be synthesized into netlists suitable for implementation on programmable devices like FPGAs or ASICs.

**12. Programming Constructs:** Verilog includes programming constructs like if, case, for, and while for control flow and conditional operations.

**13. Tasks and Functions:** Tasks and functions allow for modularization and code reuse within Verilog designs.

**14. File Types:** Verilog uses different file types, including .v for Verilog source files, .sv for System Verilog files, and others.

**15. Hierarchy:** Verilog supports hierarchical design where modules can be instantiated within other modules to create a modular and scalable design structure.

**EXPERIMENT NO – 01**

**Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates.**

**Aim:** Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates.





**Objectives:**









1. Simplify 4-variable logic expression for efficient design.
2. Simulate using basic gates for practical verification and optimization.

**Theory:****SUM OF PRODUCT:**

The short form of the sum of the product is SOP, and it is one kind of **Boolean algebra** expression. In this, the different product inputs are being added together. The product of inputs is Boolean logical AND whereas the sum or addition is Boolean logical OR. Before going to understand the concept of the sum of products

**Expression of SOP  $F=AB+C(D+E)$** 

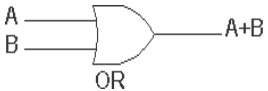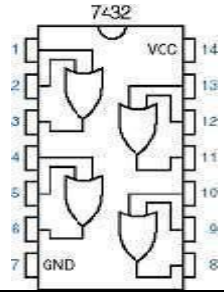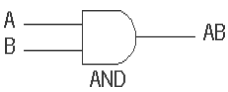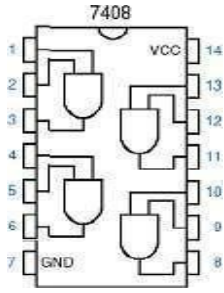Gate	Description	Truth Table			Logic Symbol	Pin Diagram
OR	The output is active high if any one of the input is in active high state, Mathematically, $Q = A+B$	A	B	Output		
		0	0	0		
		0	1	1		
		1	0	1		
		1	1	1		
AND	The output is active high only if both the inputs are in active high state, Mathematically,	A	B	Output		
		0	0	0		
		0	1	0		
		1	0	0		
		1	1	1		

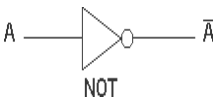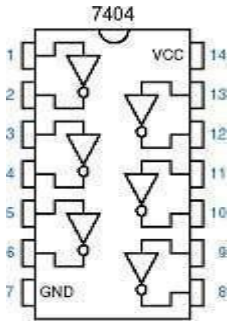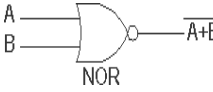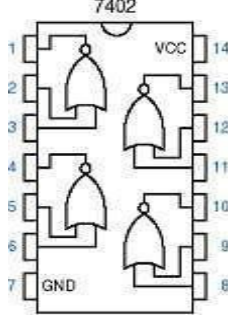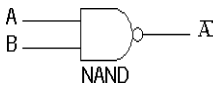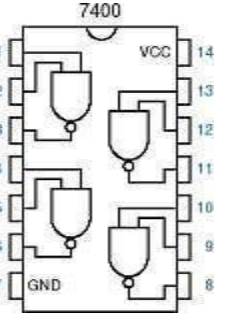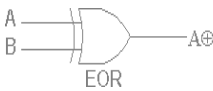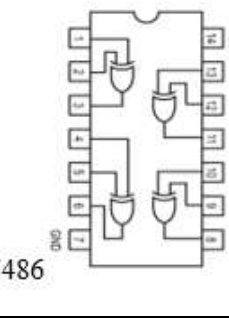NOT	In this gate the output is opposite to the input state, Mathematically, $Q = A$	A		Output		
NOR	The output is active high only if both the inputs are in active low state, Mathematically, $Q = (A+B)'$	A	B	Output		
NAND	The output is active high only if any one of the input is in active low state, Mathematically, $Q = (A.B)'$	A	B	Output		
XOR	The output is active high only if any one of the input is in active high state, Mathematically, $Q = A.B' + B.A'$	A	B	Output		

**Equipment / components required:**


- Computer with Modelsim
- HP Computer i4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Modelsim - 5.7c

**Procedure:**

1. Open Multisim software on your computer.
2. Click on "File" and select "New" to create a new schematic.
3. Drag and drop components from the component toolbar onto the workspace.
4. Connect the components using wires. Specify values and properties for components.

5. Add a power supply to the circuit. Connect it appropriately (Vcc and GND).
6. Double-click on components to open their properties.
7. Set parameters, such as resistor values, capacitor values, etc.
8. Click on "Simulate" in the toolbar.
9. Set simulation parameters like start time, stop time, and time step.
10. Add instruments to measure and observe circuit behavior.
11. Click on the "Run" button (play icon) to start the simulation.
12. Observe and analyze waveforms and measurements from the instruments. Check for correct circuit behavior.
13. If unexpected results occur, review the circuit, component values, and connections. Make necessary adjustments and rerun the simulation.
14. Save your schematic and simulation results.
15. Document the circuit design, simulation parameters, and observed behavior.
16. Export simulation results or circuit diagrams for sharing or further analysis.

### **Simulation Output:**

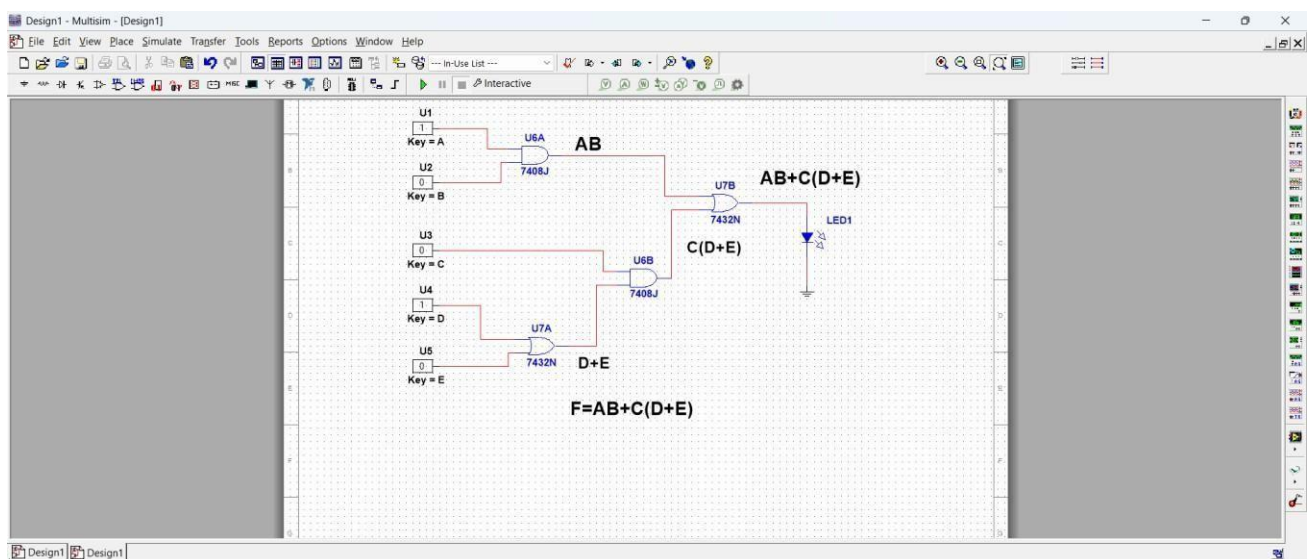

### **Results & conclusions:**

The Simulate for Given a 4-variable logic expression, simplify it using appropriate technique using basic gates are verified.

### **Possible viva questions:**

1. What is Multisim?

Answer: Multisim is a simulation software developed by National Instruments that allows users to design, simulate, and analyze electronic circuits. It provides a virtual environment for testing circuits before physical implementation

**2. How does Multisim aid in circuit design?**

Answer: Multisim allows users to create and simulate electronic circuits virtually, enabling them to test the functionality and performance of the circuits without the need for physical components. This aids in the design and validation process.

**3. What types of components can you simulate in Multisim?**

Answer: Multisim supports a wide range of electronic components, including resistors, capacitors, inductors, transistors, op-amps, microcontrollers, and more. Users can simulate both analog and digital components in their circuits.

**4. What is the purpose of simplifying a logic expression?**

Answer: Simplifying a logic expression reduces the number of gates needed, leading to more efficient and faster circuits.

**5. How many cells does a 4-variable K-map have?**

Answer: A 4-variable K-map has 16 cells ( $2^4$ ).

**6. Explain the steps involved in simplifying a Boolean expression using K-maps.**

Answer: Identify minterms, group adjacent 1s in the K-map, find the minimal sum-of-products (SOP) expression, and then apply any additional simplifications.

**7. Given a 4-variable expression  $ABCD + A'C'D + A'BD'$ , simplify it using a K-map.**

Answer: The simplified expression is  $AD' + A'C'$ .

**8. Given the expression  $(A + B)(C + D)$ , simplify it using Boolean algebra.**

Answer:  $AC + AD + BC + BD$

**9. What is the significance of don't care conditions in logic simplification?**

Answer: Don't care conditions represent input combinations for which the output value is not critical. Utilizing don't care conditions allows for further optimization during simplification.

**EXPERIMENT NO – 02**

**Design a 4 bit full adder and subtractor and simulate the same using basic gates.**


**Aim:** To design a 4 bit full adder and subtractor and simulate the same using basic gates.

**Objectives:**

1. Design a 4-bit full adder and subtractor circuit in Multisim using basic gates.
2. Simulate the circuit to analyze and verify correct functionality, considering various input scenarios.

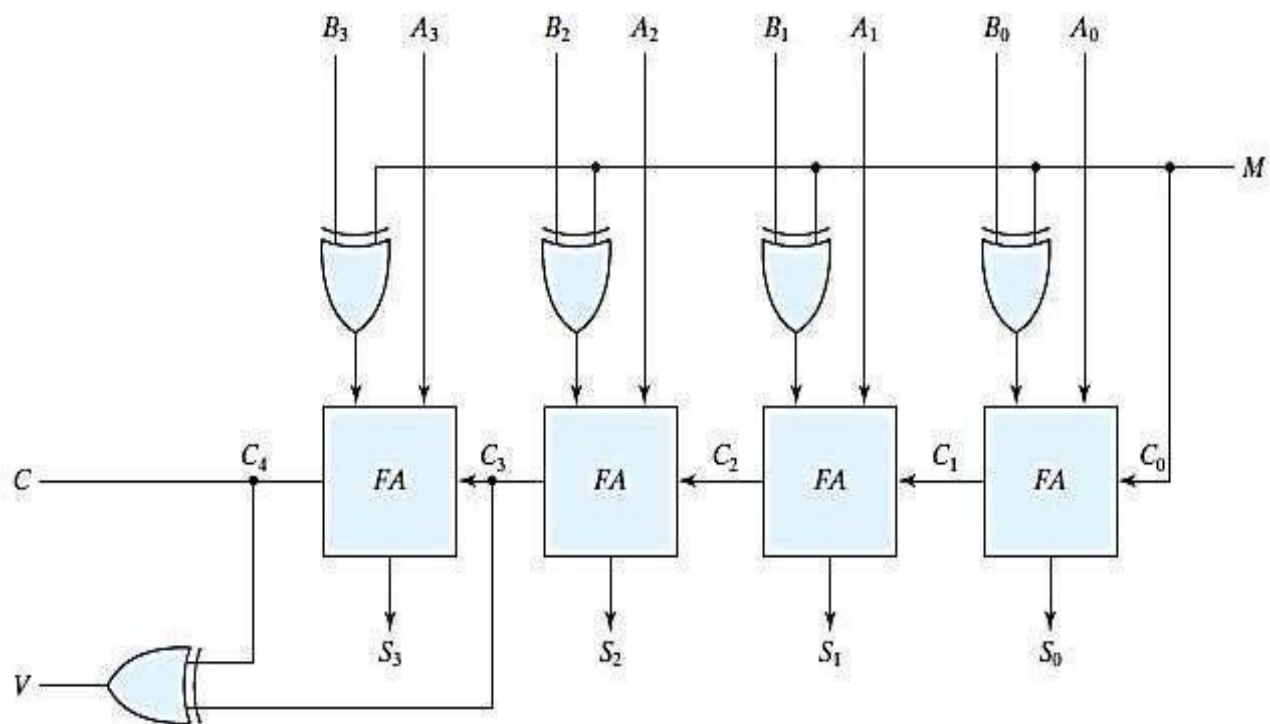**Theory:**

The addition and subtraction operations can be combined into one circuit with one common binary adder by including an exclusive-OR gate with each full-adder.



The mode input M controls the operation as the following:

If  $M=0$  → the circuit is an adder

$M=1$  → the circuit becomes a subtractor

Each exclusive-OR gate receives input M and one of the inputs of B.

- When  $M = 0$ , we have  $B \oplus 0 = B$ . The full adders receive the value of B, the input carry is  $C_0 = 0$ , and the circuit performs  $A + B$ .

- When  $M = 1$ , we have  $B \oplus 1 = \bar{B}$  and  $C_0 = 1$ . The B inputs are all complemented and a 1 is added through the input carry. The circuit performs the operation  $A + (\text{the 2's complement of } B) = A - B$
- The exclusive-OR with output V is for detecting an overflow.

The binary adder-subtractor circuit with outputs C and V is shown in Fig. 4.13. If the two binary numbers are considered to be unsigned, then the C bit detects a carry after addition or a borrow after subtraction. If the numbers are considered to be signed, then the V bit detects an overflow. If  $V = 0$  after an addition or subtraction, then no overflow occurred and the n-bit result is correct. If  $V = 1$ , then the result of the operation contains  $n + 1$  bits, but only the rightmost n bits of the number fit in the space available, so an overflow has occurred. The  $1n + 12$ th bit is the actual sign and has been shifted out of position.




### **Equipment / components required:**

- Computer with Modelsim
- HP Computer i4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Modelsim - 5.7c


### **Procedure / activity:**

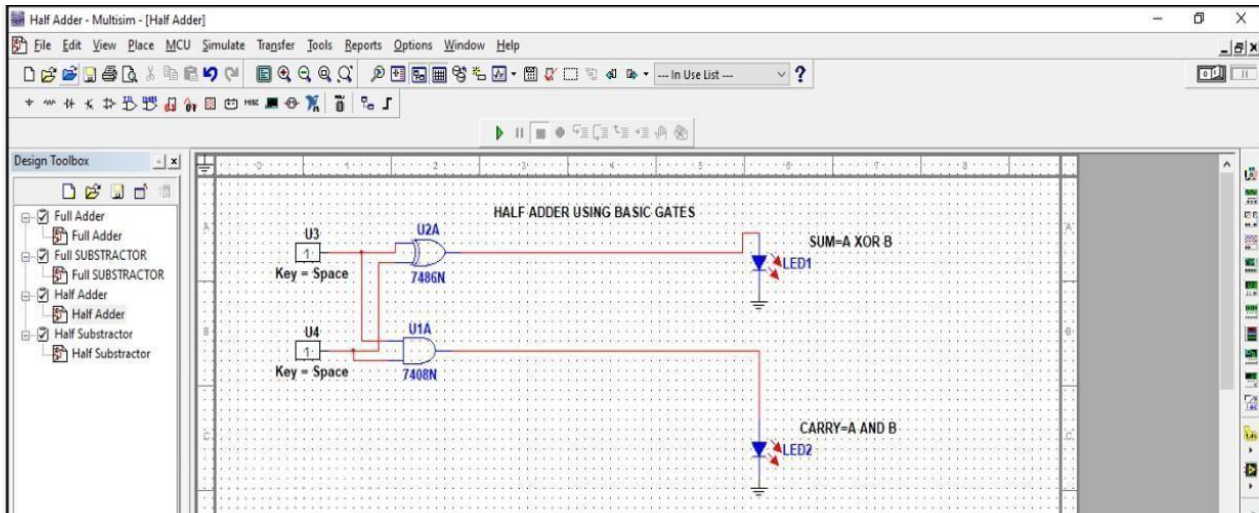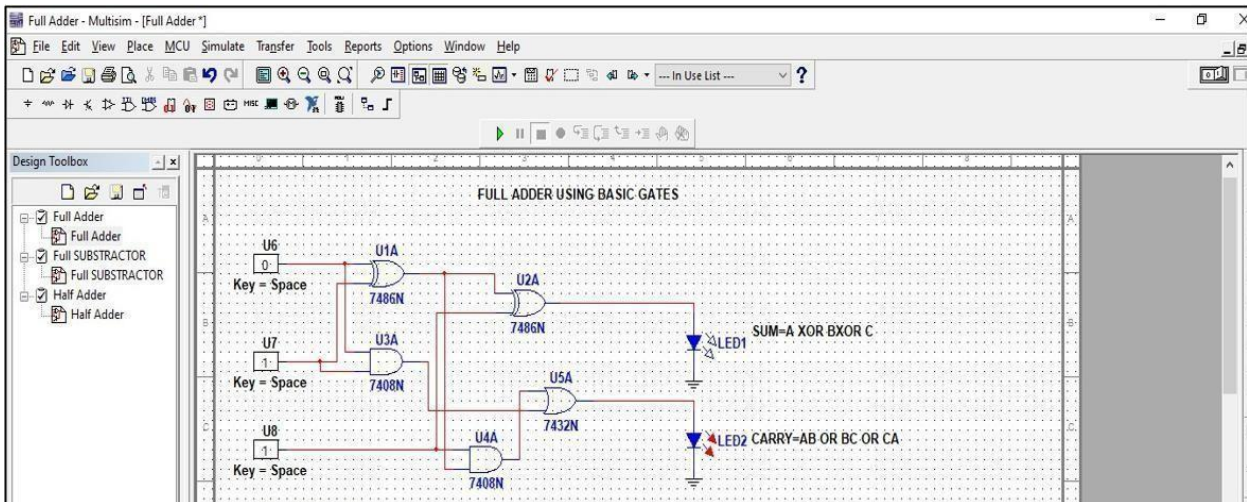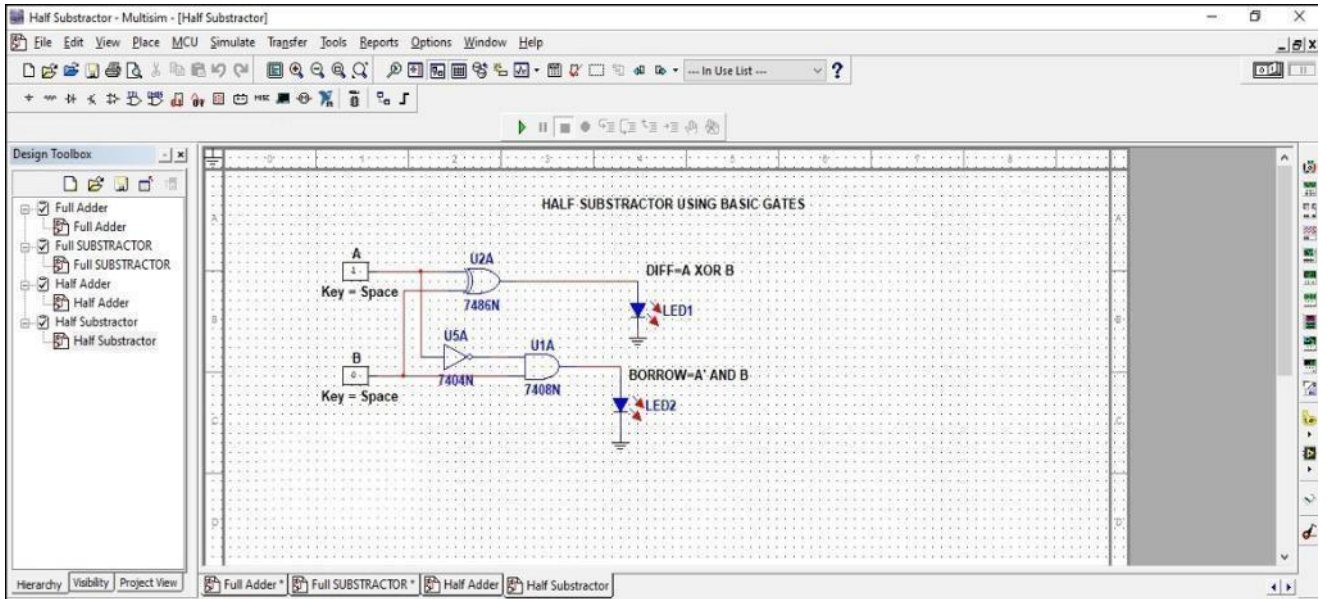1. Open Multisim software on your computer.
2. Click on "File" and select "New" to create a new schematic.
3. Drag and drop components from the component toolbar onto the workspace.
4. Connect the components using wires. Specify values and properties for components.
5. Add a power supply to the circuit. Connect it appropriately ( $V_{cc}$  and GND).
6. Double-click on components to open their properties.
7. Set parameters, such as resistor values, capacitor values, etc.
8. Click on "Simulate" in the toolbar.
9. Set simulation parameters like start time, stop time, and time step.
10. Add instruments to measure and observe circuit behavior.
11. Click on the "Run" button (play icon) to start the simulation.
12. Observe and analyze waveforms and measurements from the instruments. Check for correct circuit behavior.
13. If unexpected results occur, review the circuit, component values, and connections. Make necessary adjustments and rerun the simulation.
14. Save your schematic and simulation results.
15. Document the circuit design, simulation parameters, and observed behavior.
16. Export simulation results or circuit diagrams for sharing or further analysis.




**Simulation Output:****HALF ADDER****FULL ADDER****HALF SUBTRACTOR**

## FULL SUBTRACTOR

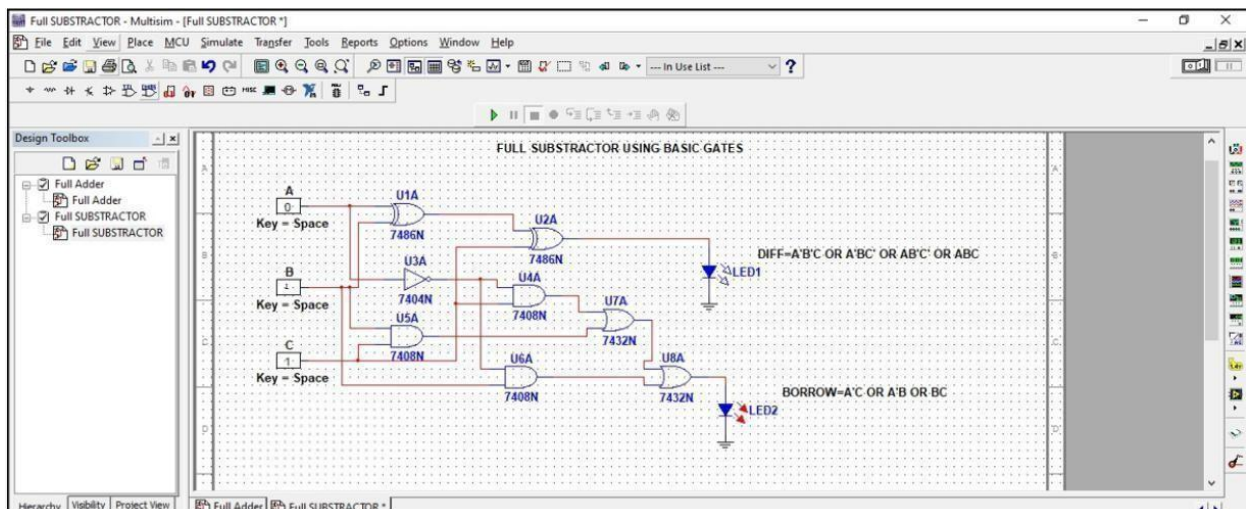

## 4-BIT ADDER & SUBTRACTOR

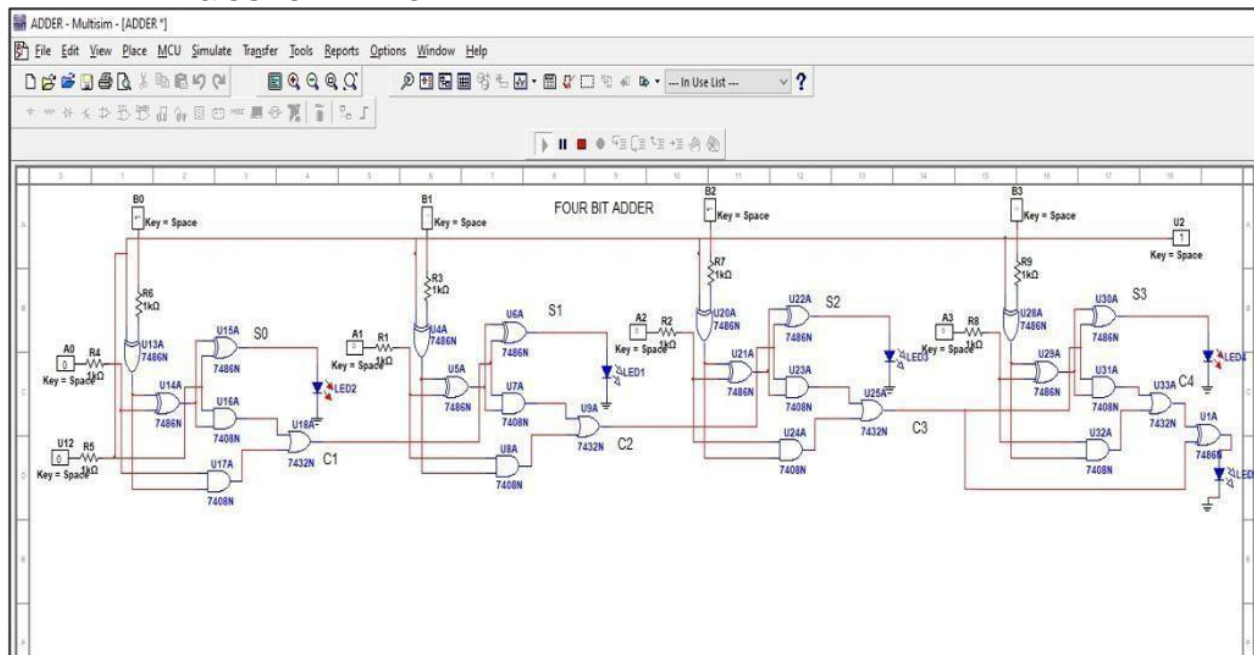

**Results & conclusions:** Simulated 4-bit full adder and subtractor in Multisim, verified correct outputs, efficient gate use, and stable performance. Achieved accurate, optimized, and versatile circuit design.

### Possible viva questions:

- What is the primary function of a 4-bit full adder?**  
A 4-bit full adder performs addition on two 4-bit binary numbers, considering inputs and generating a sum along with a carry-out.
- Can a 4-bit full adder handle subtraction as well?**  
Yes, a 4-bit full adder can be used for subtraction by incorporating additional logic to manage borrow inputs and adjustments.
- How many control inputs are there in a 4-bit full subtractor for each XOR gate used?**

**4. What is the purpose of the AND gates in a full subtractor?**

- A) Generate the sum output
- B) Generate the borrow-out
- C) Perform bitwise AND operation
- D) Implement overflow detection

Answer: C) Perform bitwise AND operation

**5. List the basic gates required to design a 4-bit full adder.**

Answer: Basic gates include AND gates, XOR gates, and OR gates.

**6. In a 4-bit full subtractor, what is the role of the borrow-out?**

- A) It indicates a borrow to the next stage.
- B) It determines the most significant bit of the difference.
- C) It controls the XOR gates.
- D) It is not used in subtraction.

Answer: A) It indicates a borrow to the next stage.

**7. What is the purpose of the AND gates in a full subtractor?**

- A) Generate the sum output
- B) Generate the borrow-out
- C) Perform bitwise AND operation
- D) Implement overflow detection

Answer: C) Perform bitwise AND operation

**8. How would you simulate the 4-bit full adder and subtractor using basic gates in a software tool like Multisim or similar?**

Answer: Create a schematic in the simulation tool, instantiate the required basic gates (AND, XOR, OR), and interconnect them according to the design of the 4-bit full adder and subtractor. Apply appropriate inputs and observe the outputs.

**9. How many XOR gates are required for the sum output in a 4-bit full adder?**

Answer: Four XOR gates are required for generating the sum outputs in a 4-bit full adder.

**10. Can you identify any challenges or considerations when designing a 4-bit full subtractor?**

Answer: One consideration is managing borrow inputs for each bit subtraction, and careful handling of borrow propagation to ensure accurate subtraction results.

**EXPERIMENT NO – 03****Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.**


**Aim:** To design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.

**Objectives:**

1. Implement Verilog for simple circuits using structural, data flow, and behavioral models.
2. Verify designs through simulation for functionality and performance assessment.

**Theory:**

As mentioned previously, the module is the basic building block for modeling hardware with the Verilog HDL. The logic of a module can be described in anyone (or a combination) of the following modeling styles:

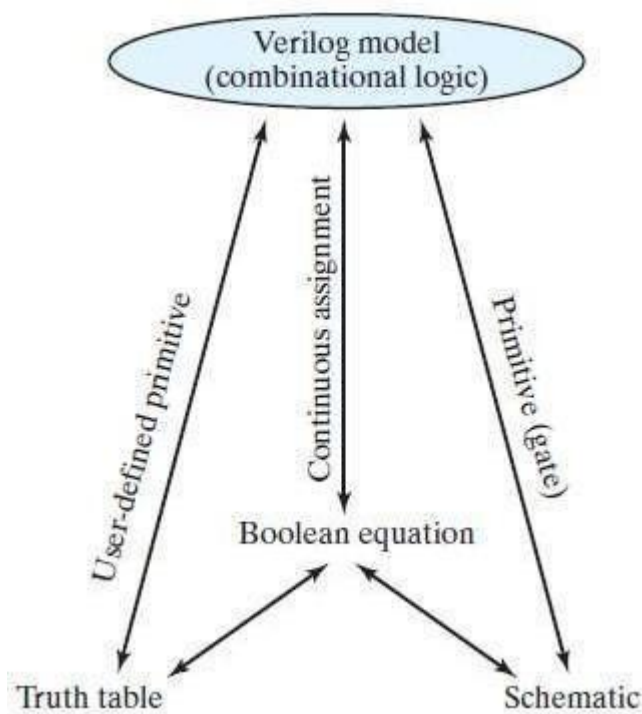

**FIGURE 3.1: Relationship of Verilog constructs to truth tables, Boolean equations, and schematics**

- **Gate-level modeling** using instantiations of predefined and user-defined primitive gates.
  - Gate-level (structural) modeling describes a circuit by specifying its gates and how they are connected with each other.



- **Dataflow modeling** using continuous assignment statements with the keyword assign.
  - Dataflow modeling is used mostly for describing the Boolean equations of combinational logic.
- **Behavioral modeling** using procedural assignment statements with the keyword always.
  - behavioral modeling that is used to describe combinational and sequential circuits at a higher level of abstraction.

Combinational logic can be designed with truth tables, Boolean equations, and schematics; Verilog has a construct corresponding to each of these “classical” approaches to design: user-defined primitives, continuous assignments, and primitives, as shown in Fig. 3.1. There is one other modeling style, called switch-level modeling. It is sometimes used in the simulation of MOS transistor circuit models, but not in logic synthesis. We will not consider switch-level modeling.

### **Equipment / components required:**

- Computer with Modelsim Software Specifications:
- HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Modelsim - 5.7c, Xilinx - 14.1i.

### **Procedure / activity:**


1. Open a Model Sim IDE.
2. Create a new project through the project navigator icon.
3. Add Verilog new source to the project depending on the user requirement.
4. Select the Verilog HDL mode.
5. Assign the inputs and outputs for the system to design.
6. And write the code as given below for the functionality.
7. Synthesize the code and correct the syntax errors if any.
8. Isim Simulator and Behavioral check syntax the Simulation.
9. Observe the output timing waveform and verify it with the truth table.

### **Verilog code:**

<b>Structural-</b>	<b>Data Flow-</b>	<b>Behavioural Model-</b>
<pre> module logicg(a, b,y0,y1,y2,y3,y4,y5,y6); input a,b; output y0,y1,y2,y3,y4,y5,y6; not g1(y0,a); and g2(y1,a,b); or g3(y2,a,b); nand g4(y3,a,b); nor g5(y4,a,b); xor g6(y5,a,b); xnor g7(y6,a,b); endmodule </pre>	<pre> module ldataflow(a, b,y0,y1,y2,y3,y4,y5,y6); input a,b; output y0,y1,y2,y3,y4,y5,y6;     assign y0=!a;     assign y1=a&amp;b;     assign y2=a b;     assign y3=!(a&amp;b);     assign y4=!(a b);     assign y5=a^b;     assign y6=!(a^b); endmodule </pre>	<pre> module      logicgB(a, b,y0,y1,y2,y3,y4,y5,y6);     input a,b; output y0,y1,y2,y3,y4,y5,y6; reg y0; reg y1; reg y2; reg y3; reg y4; reg y5; reg y6; always @(a,b) </pre>

		<pre> begin y0=!a; y1=a&amp;b; y2=a b; y3=!(a&amp;b); y4=!(a b); y5=a^b; y6=!(a^b); end endmodule </pre>
--	--	--

### Simulation Output:

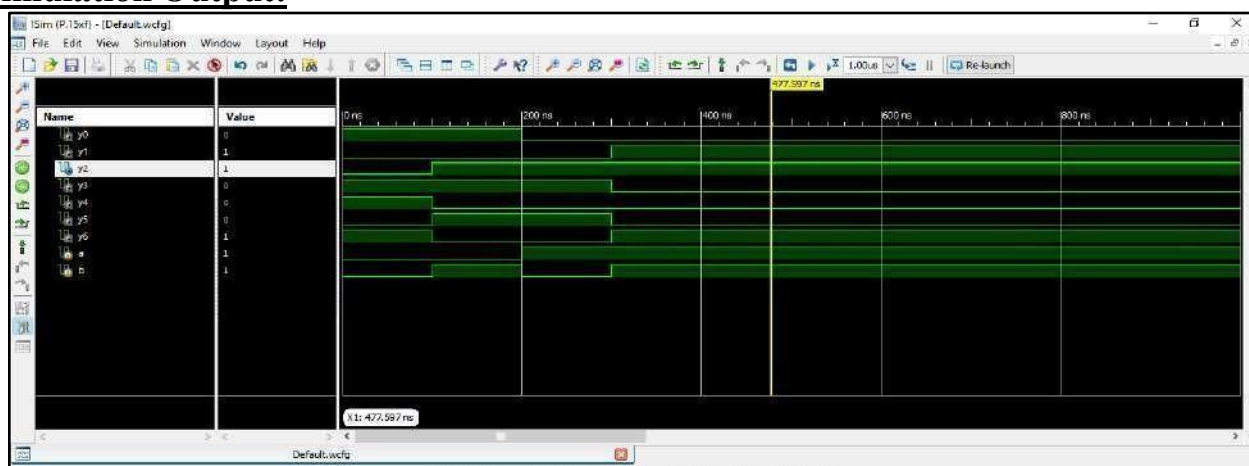

**Results & conclusions:** The Verilog code for simple circuits using structural, Data flow and Behavioral model are verified.

### Possible viva questions:

#### 1. What is Verilog HDL?

Verilog Hardware Description Language (HDL) is a language used for modeling electronic systems at the behavioral and structural levels, commonly employed in digital design and simulation.

#### 2. Explain the structural modeling in Verilog.

Structural modeling involves building circuits using predefined modules. Instances of modules are interconnected to create a complete design.

#### 3. Explain the concept of continuous assignment in data flow modeling.

Continuous assignments use the assign keyword to express the relationship between signals. These assignments operate continuously, updating the output whenever input signals change.

#### 4. In behavioral modeling, what does the always block signify?

The always block in behavioral modeling defines a set of conditions and statements that are executed whenever the conditions specified in the sensitivity list change.

#### 5. Can Verilog be used for both simulation and synthesis?

Yes, Verilog is versatile and can be used for both simulations, to verify designs, and synthesis, to generate hardware based on the design description

**6. How are signals represented in behavioral modeling in Verilog?**

In behavioral modeling, signals are represented using variables and expressions. Changes in variables trigger the execution of blocks, simulating the algorithmic behavior.

**7. How is time accounted for in behavioral modeling in Verilog?**

Behavioral modeling can include delays using constructs like # to represent time delays between statements. This allows simulation to account for time-dependent behavior.

**8. How does structural modeling differ from behavioral modeling in Verilog?**

Structural modeling focuses on the interconnection of modules, representing the physical structure of the circuit. Behavioral modeling emphasizes the algorithmic functionality, abstracting the physical implementation details.

**9. In which scenarios would you prefer to use structural modeling in Verilog?**

Structural modeling is beneficial when designing circuits with well-defined modules and known physical implementations, making it suitable for hierarchical designs.

**10. When is behavioral modeling more appropriate in Verilog?**

Behavioral modeling is preferred for abstractly describing the functionality of a circuit without concern for the specific physical structure. It is useful for algorithmic or higher-level design descriptions.

---

**EXPERIMENT NO – 04****Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.**

**Aim:** To Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.

**Objectives:**

1. Create Verilog HDL for Binary Adder-Subtractor, including Half and Full Adder, Half and Full Subtractor.
2. Validate functionality through simulation for accurate arithmetic operations in digital systems.

**Theory:**

**Adder** is a combinational digital circuit that is used for adding two numbers. A typical adder circuit produces a sum bit (denoted by S) and a carry bit (denoted by C) as the output. Adder circuits are of two types: Half adder and Full adder.

Half-Adder: A combinational logic circuit that performs the addition of two data bits, A and B, is called a half-adder. Addition will result in two output bits; one of which is the sum bit, S, and the other is the carry bit, C.

Full-Adder: The half-adder does not take the carry bit from its previous stage into account. This carry bit from its previous stage is called carry-in bit. A combinational logic circuit that adds two data bits, A and B, and a carry-in bit  $C_{in}$ , is called a full-adder.

**Subtractor** is a combinational digital circuit that is used for subtracting two numbers. A typical subtractor circuit produces a diff bit (denoted by D) and a borrow bit (denoted by B) as the output. Subtractor circuits are of two types: Half subtractor and Full subtractor.

Half Subtractor: A combinational logic circuit that performs the subtraction of two data bits, A and B, is called a half-adder. Subtraction will result in two output bits; one of which is the diff bit, D, and the other is the borrow bit, B.

Full Subtractor: A combinational logic circuit that subtracts two data bits, A and B and a borrow in bit, is called full subtractor.



## Using Basic Gates


### Half Adder

Half Adder

Input		output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = \overline{A}B + A\overline{B}$$

$$\text{Carry} = AB$$

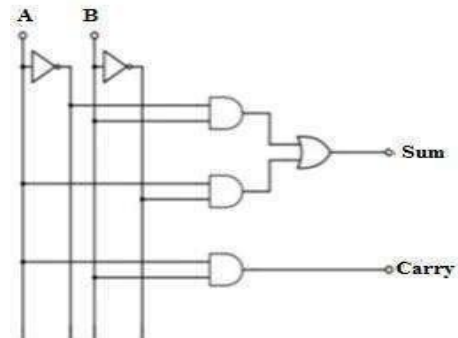


### Half Subtractor

Input		output	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Difference} = \overline{A}B + A\overline{B}$$

$$\text{Borrow} = \overline{A}B$$

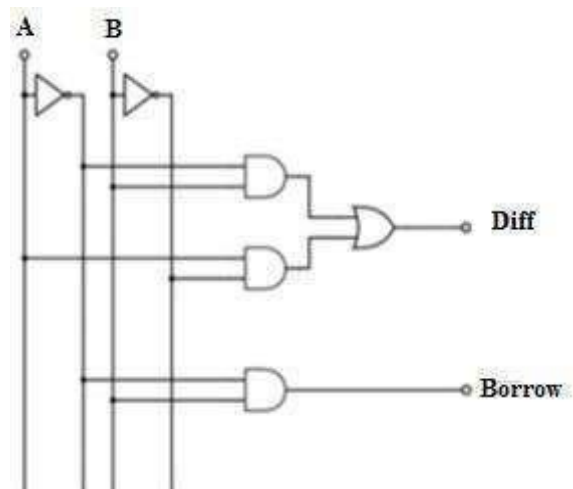


### Full Adder

Full adder

Input			output	
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = \overline{a}\overline{b}c + \overline{a}b\overline{c} + a\overline{b}\overline{c} + ab\overline{c}$$
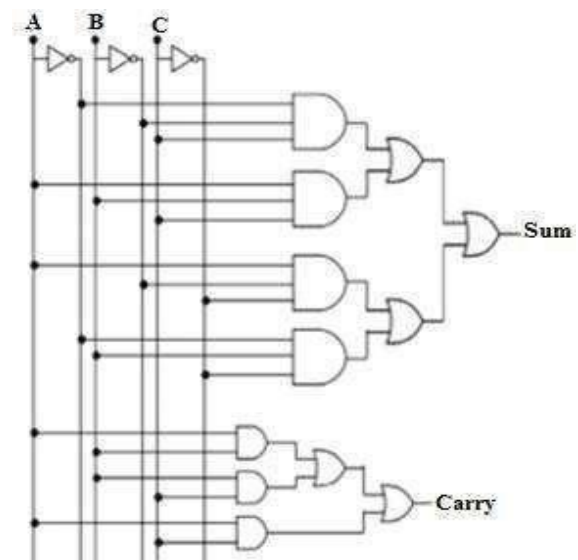
$$\text{Carry} = a\overline{b} + a\overline{c} + b\overline{c}$$




## Full Subtractor

Full Subtractor

Input			output	
A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$\text{Difference} = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$
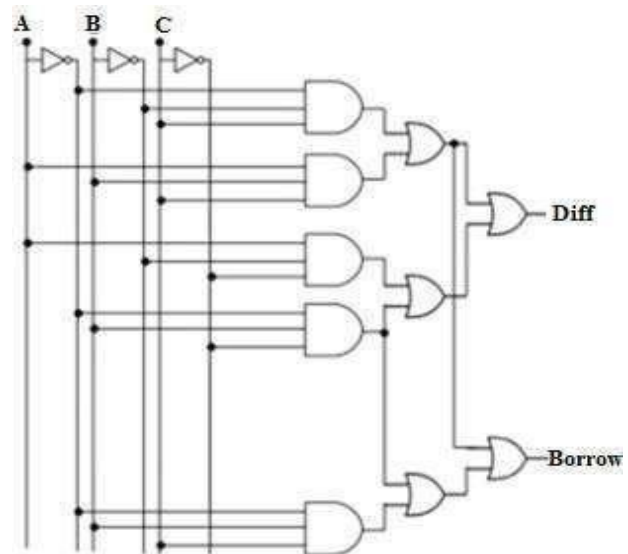
$$\text{Borrow} = \bar{a}c + \bar{a}b + bc$$



### Using EX-OR Gates


#### Half Adder

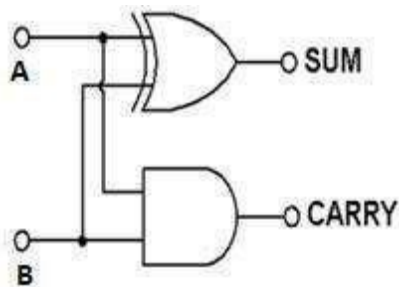

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = AB$$


#### Half Subtractor

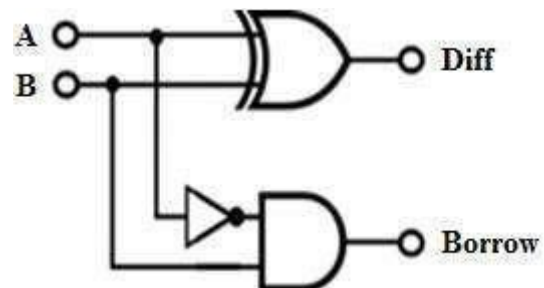

$$\text{Diff} = A \oplus B$$

$$\text{Borrow} = A'B$$


#### Full Adder

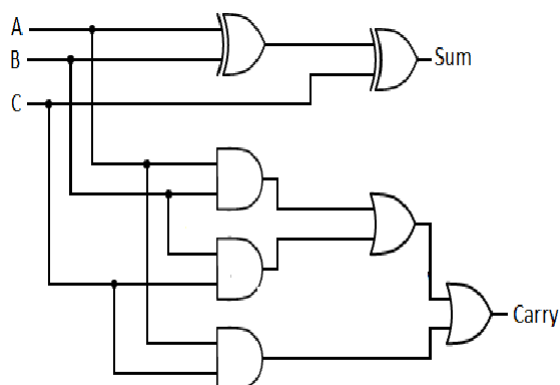

$$\text{Sum} = A \oplus B \oplus C$$

$$\text{Carry} = AB + BC + AC$$

#### Full Subtractor

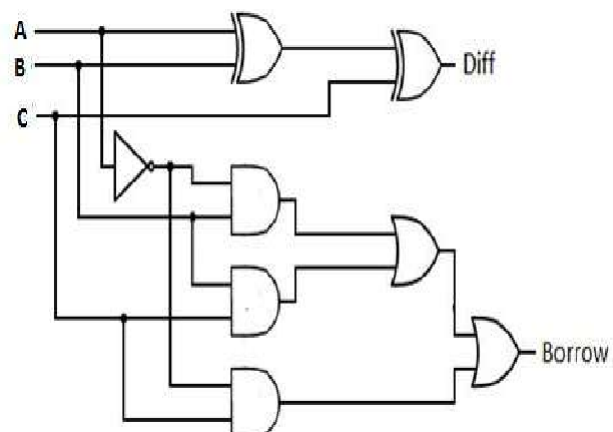

$$\text{Diff} = A \oplus B \oplus C$$

$$\text{Borrow} = A'B + BC + A'C$$

**Equipment / components required:**


- Computer with Modelsim Software Specifications:
- HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Modelsim - 5.7c, Xilinx - 14.1i.

**Procedure / activity:**


1. Open a Model Sim IDE.
2. Create a new project through the project navigator icon.
3. Add Verilog new source to the project depending on the user requirement.
4. Select the Verilog HDL mode.
5. Assign the inputs and outputs for the system to design.
6. And write the code as given below for the functionality.
7. Synthesize the code and correct the syntax errors if any.
8. Isim Simulator and Behavioral check syntax the Simulation.
9. Observe the output timing waveform and verify it with the truth table.

**Verilog code:**


Half Adder-	Half Subtractor-
<pre>module halfadder(a,b,sum,carry);   input a,b;   output sum,carry;   assign sum=a^b;   assign carry=a&amp;b; endmodule</pre>	<pre>module HS(a,b,diff,borrow);   input a,b;   output diff,borrow;   assign diff=a^b;   assign borrow=!a&amp;b; endmodule</pre>
Full Adder-	Full Subtractor-
<pre>module FA(a,b,c,sum,carry);   input a,b,c;   output sum,carry;   assign sum=a^b^c;   assign carry=(a&amp;b)  b&amp;c  (c&amp;a); endmodule</pre>	<pre>module FS(a,b,c,diff,borrow);   input a,b,c;   output diff,borrow;   assign diff=a^b^c;   assign borrow=((!a)&amp;b)  b&amp;c  (c&amp;!a); endmodule</pre>

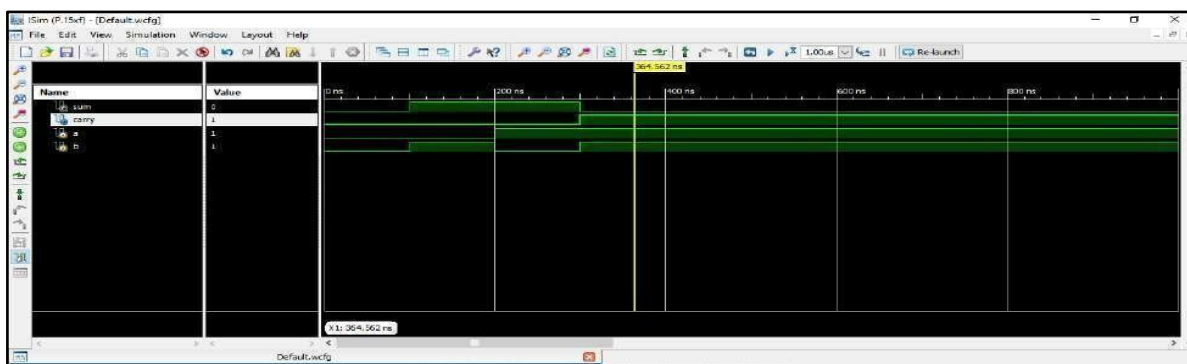**Simulation Output:****Half Adder-**


### Half Subtractor-

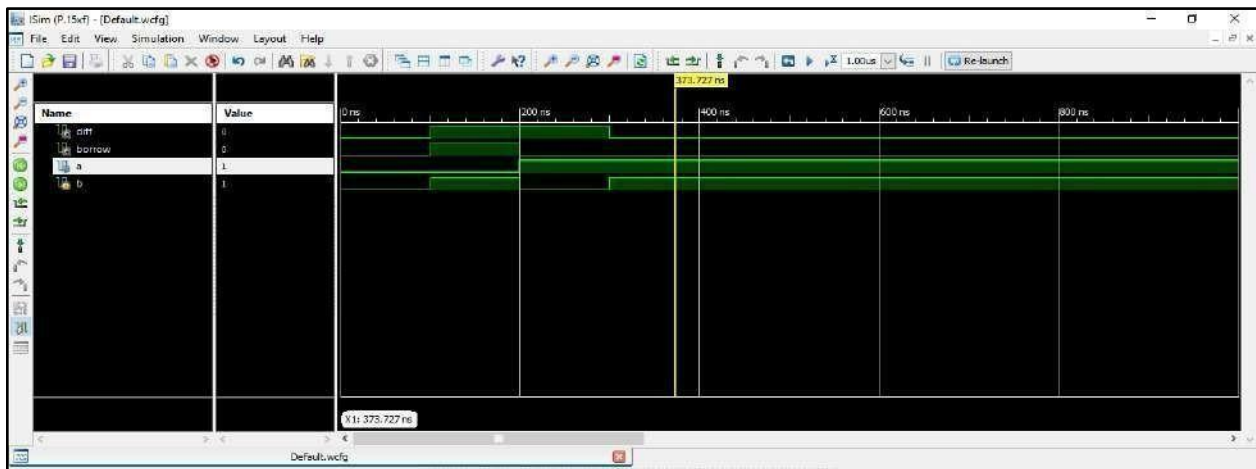

### Full Adder-

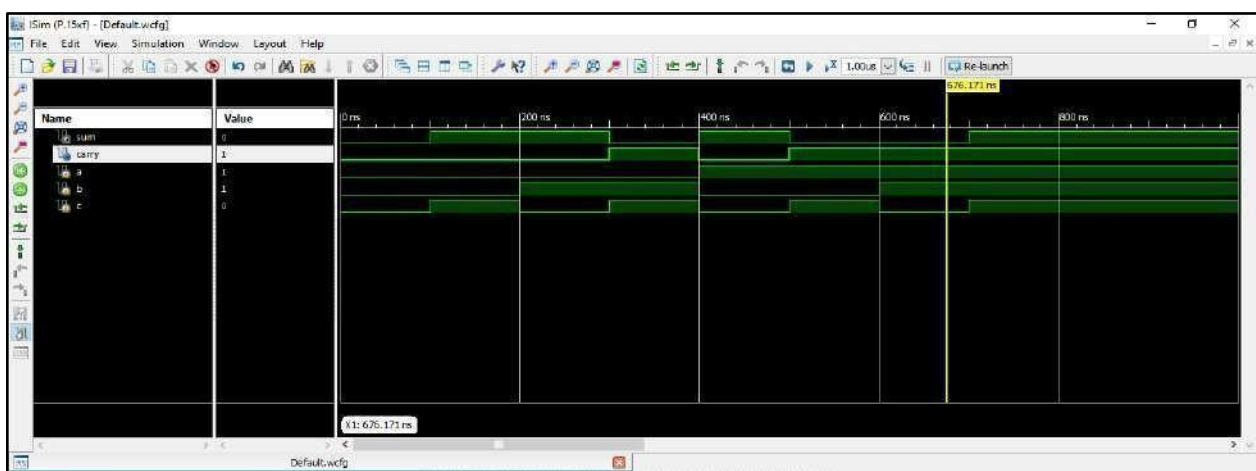

### Full Subtractor

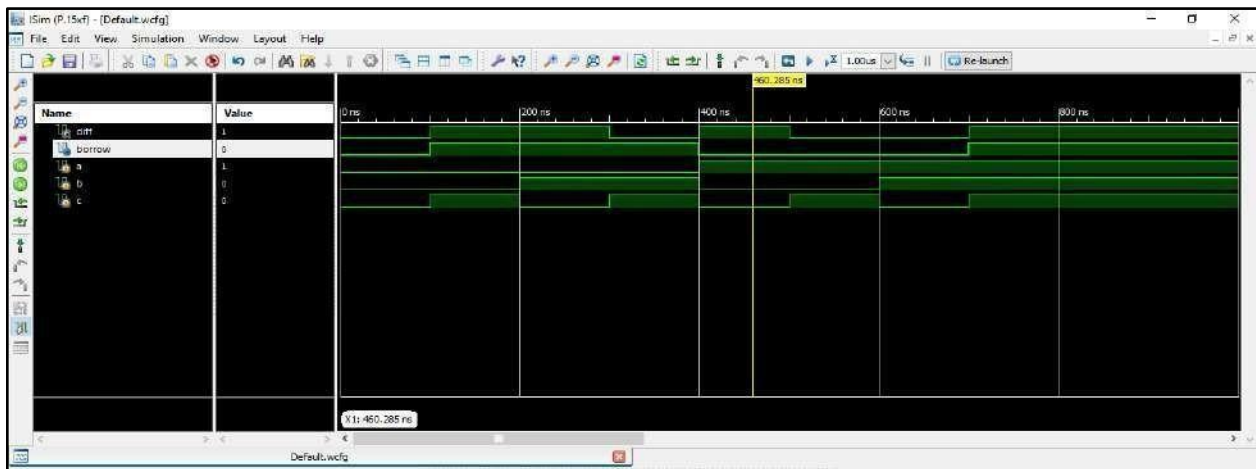

**Results & conclusions:** The Verilog code for adders and subtractors are verified.

### Possible viva questions:

1. What is the basic function of a binary adder?

**Ans:** A binary adder combines two binary numbers, producing their sum and a possible carry output.

**2. What is a Half Adder in binary arithmetic?**

**Ans:** A Half Adder adds two binary digits (bits) and produces a sum and a carry-out. It lacks the ability to handle a carry-in from a previous stage.

**3. How does a Full Adder differ from a Half Adder?**

**Ans:** A Full Adder adds three binary digits (two inputs and a carry-in) to produce a sum and a carry-out, enabling it to handle carry inputs from previous stages.

**4. What is a Half Subtractor in binary arithmetic?**

**Ans:** A Half Subtractor subtracts two binary digits and produces a difference and a borrow-out. It does not consider borrow inputs from previous stages.

**5. How does a Full Subtractor differ from a Half Subtractor?**

**Ans:** A Full Subtractor subtracts three binary digits (two inputs and a borrow-in) to produce a difference and a borrow-out. It can handle borrow inputs from previous stages.

**6. How does a Half Subtractor handle the case when the minuend is smaller than the subtrahend?**

**Ans:** In such cases, the Half Subtractor produces a difference without a borrow-out, signifying that no borrowing is required for the subtraction.

**7. Explain the significance of the carry-in and borrow-in signals in Full Adders and Full Subtractors.**

**Ans:** The carry-in (Cin) in Full Adders and the borrow-in in Full Subtractors represent inputs from the previous stage, allowing these circuits to operate on multiple bits.

**8. Can a Full Subtractor be constructed using Half Subtractors?**

**Ans:** Yes, a Full Subtractor can be built using two Half Subtractors and additional logic to manage borrow inputs.

**9. How does the carry propagation differ in Adders and Subtractors?**

**Ans:** In Adders, carries propagate from lower bits to higher bits during addition, while in Subtractors, borrows propagate from higher bits to lower bits during subtraction.

**10. Why is it called a "Half" Adder or Subtractor?**

**Ans:** It is called "Half" because it handles only two input bits, not considering any carry or borrow inputs from previous stages, making it a simpler building block compared to "Full" Adders and Subtractors.

**EXPERIMENT NO – 05****Design Verilog HDL to implement Decimal adder**

**Aim:** To Design Verilog HDL to implement Decimal adder.

**Theory:** BCD or Binary coded decimal is a way of representing decimal digits in binary form.

Generally 4 bits are used to represent values 0 to 9.

Decimal Digit	BCD 8 4 2 1
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0

Decimal Digit	BCD 8 4 2 1
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1

A BCD adder, takes in two BCD numbers as inputs, and outputs a BCD digit along with a carry output. If the sum of the BCD digits is less than or equal to 9, then we don't have a problem. But if its greater than 9, we have to convert it into BCD format. This is done by adding 6 to the sum and taking only the least significant 4 bits. The MSB bit is output as carry.

Consider the below BCD addition:

$$1001 + 1000 = 10001$$

$$9 + 8 = 17$$

The output 17 is more than 9. So we add 6 to it. So we get,

$$17+6 = 23 \text{ (in binary 23 is 10111)}$$

Now the least significant 4 bits (which is "0111") represent the units digit and the MSB(4th bit which is '1') bit represents the tens digit. Since the range of input is 0 to 9, the maximum output is 18. If you consider a carry it becomes 19. This means at the output side we need a 4 bit sum and a 1 bit carry to represent the most significant digit. These binary numbers are listed below


The condition for a correction and an output carry can be expressed by the Boolean Function

$$C = K + Z_8Z_4 + Z_8Z_2$$

When  $C = 1$ , it is necessary to add 0110 to the binary sum and provide an output carry for the next stage. A BCD adder that adds two BCD digits and produces a sum digit in BCD is shown in Figure below.

Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

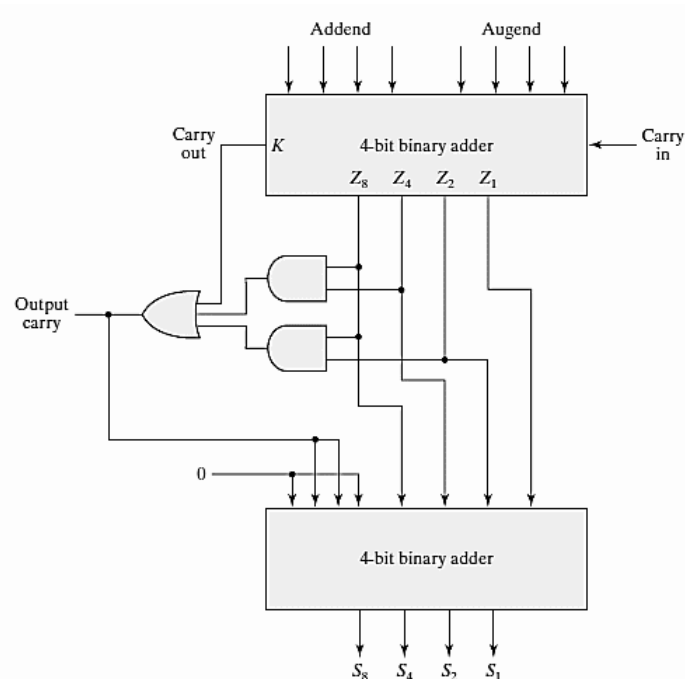**Logic Diagram:**

For multiple digit addition, you can connect the carry\_out to the carry input of the next adder. A simple cascading network of these small adders is enough to realize the multiple digit BCD addition.

**Equipment:**

- Computer with Modelsim Software Specifications:
- HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Modelsim - 5.7c, Xilinx - 14.1i.

**Procedure:**

1. Open a Model Sim IDE.
2. Create a new project through the project navigator icon.


3. Add Verilog new source to the project depending on the user requirement.
4. Select the Verilog HDL mode.
5. Assign the inputs and outputs for the system to design.
6. And write the code as given below for the functionality.
7. Synthesize the code and correct the syntax errors if any.
8. Isim Simulator and Behavioral check syntax the Simulation.
9. Observe the output timing waveform and verify it with the truth table.
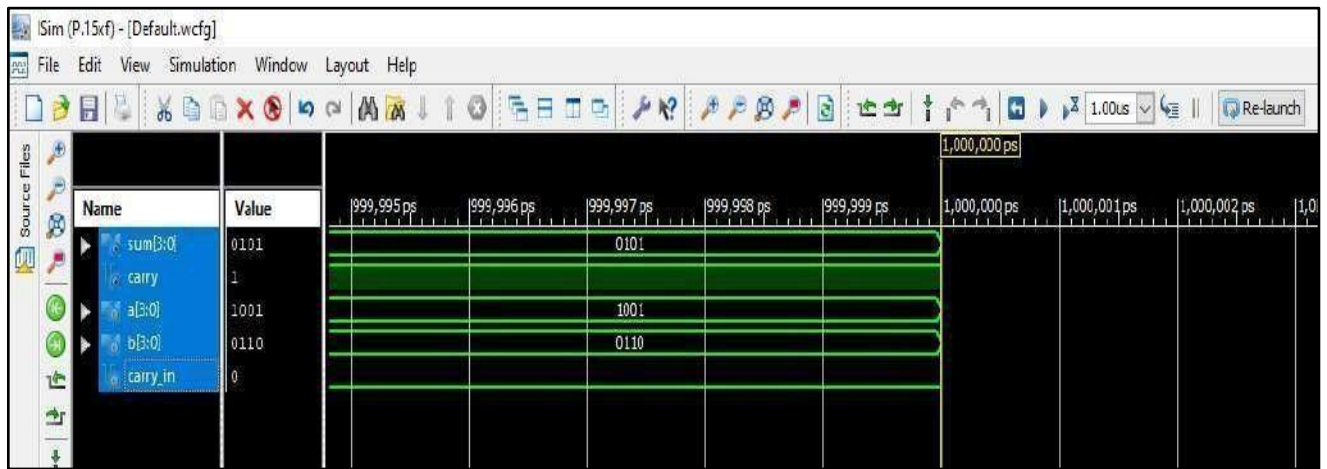
### **Verilog code for BCD addition-Behavioral level:**

```
module deciadder(a,b,carry_in,sum,carry);
input [3:0] a,b;           //declare the inputs and outputs of the module with their sizes.
input carry_in;
output [3:0] sum;
output carry;
//Internal variables
reg [4:0] sum_temp;
reg [3:0] sum;
reg carry;
//always block for doing the addition
always @(a,b,carry_in)
begin
    sum_temp = a+b+carry_in;    //add all the inputs

    if(sum_temp > 9)
        begin
            sum_temp = sum_temp+6;
            carry = 1; //set the carry output
            sum = sum_temp[3:0];
        end
    else
        begin
            carry = 0;
            sum = sum_temp[3:0];
        end
    end
end
endmodule
```



**Simulation waveform:**

**Results & conclusions:** The Verilog code for Decimal adder is simulated and verified. \_

**Possible viva questions:****1. What is a decimal adder?**

**Ans:** A decimal adder is a digital circuit designed to perform addition operations specifically for decimal numbers.

**2. How does a decimal adder differ from a binary adder?**

**Ans:** While binary adders operate on binary numbers, decimal adders process numbers in base-10, considering the decimal digits 0 through 9.

**3. Explain the significance of a carry in a decimal adder.**

**Ans:** In a decimal adder, a carry occurs when the sum of two digits exceeds 9, requiring an additional unit to be carried to the next higher decimal place.

**4. How is overflow handled in a decimal adder?**

**Ans:** Overflow occurs when the sum in a decimal place exceeds 9. In such cases, the carry is propagated to the next higher decimal place to prevent data loss.

**5. Explain the role of the carry-out in a decimal adder.**

**Ans:** The carry-out signal indicates whether there is a carry from the most significant digit (MSD), signaling potential overflow in multi-digit decimal additions.

**6. How is subtraction implemented in a decimal adder circuit?**

Subtraction in a decimal adder is achieved by using additional logic to complement and adjust the inputs based on the borrow generated during the subtraction process.

**7. Can a decimal adder handle negative decimal numbers?**

Yes, by incorporating logic to manage sign bits and handling subtraction appropriately, a decimal adder can process negative decimal numbers.

**EXPERIMENT NO – 06****Design Verilog program to implement Different types of multiplexers like 2:1, 4:1 and 8:1.**


**Aim:** Design Verilog program to implement Different types of multiplexers like 2:1, 4:1 and 8:1.

**Objectives:**

1. Develop Verilog program for 2:1, 4:1, 8:1 multiplexer design.
2. Validate through simulation for accuracy and efficiency in circuit implementation.

**Theory:**

- A multiplexer (or data selector, abbreviated as MUX) has a group of data inputs ( $2^n$ ) and a group of control inputs ( $n$ ) (also called as select inputs).
- The control inputs are used to select one of the data inputs and connect it to the output terminal.

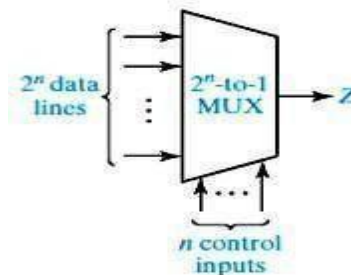


**Figure 6.1: General block diagram of  $2^n : 1$  multiplexer**

- A general block diagram of  $2^n : 1$  multiplexer is shown in the fig.3.6.
- A 2 to 1 multiplexer requires 1 select input, 4 to 1 multiplexer require 2 select inputs and 8 to 1 multiplexer require 3 select inputs.

**2:1 Multiplexer**

- A 2 to 1 multiplexer has 2 data inputs, 1 select input and 1 output.

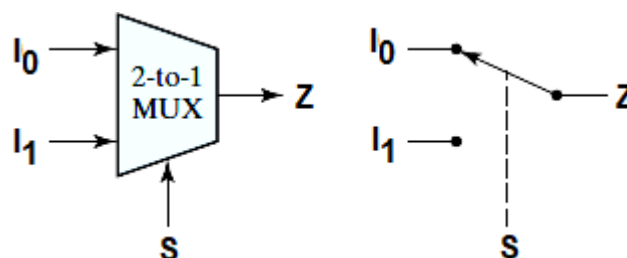

**Figure 6.2: 2 to 1 Multiplexer and Switch Analog**


- When the select (control) input A is 0, the switch is in the upper position and the MUX output is  $Z = I_0$ .
- When the select (control) input A is 1, the switch is in the lower position and the MUX output is  $Z = I_1$ .
- In other words, a MUX acts like a switch that selects one of the data inputs ( $I_0$  or  $I_1$ ) and transmits it to the output.

**Truth Table:**


Select (S)	Output (Z)
0	$I_0$
1	$I_1$

- The logic equation for the 2-to-1 MUX can be written as:

$$Z = \bar{S}I_0 + SI_1$$

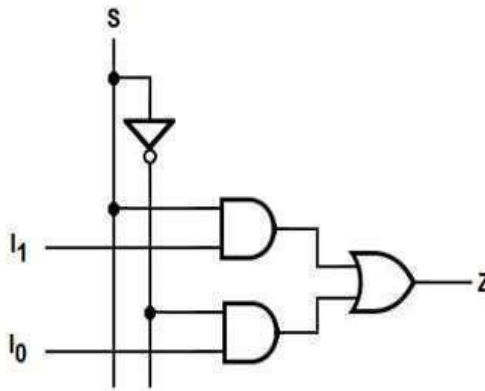**Logic Diagram:****Figure 6.3: Logic diagram of 2:1 Multiplexer****4:1 Multiplexer**

- A 4 to 1 multiplexer has 4 data inputs, 2 select inputs and 1 output.
- The 4 to 1 MUX acts like a four-position switch that transmits one of the four inputs to the output.

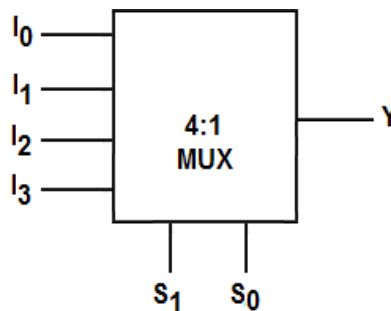**Figure 6.4: 4 to 1 Multiplexer**


- Two select (control) inputs ( $S_1$  and  $S_0$ ) are needed to select one of the four inputs. If the control inputs are  $S_1S_0 = 00$ , the output is  $I_0$ ; similarly, for the control inputs 01, 10, and 11 give outputs of  $I_1$ ,  $I_2$ , and  $I_3$ , respectively.

**Truth Table:**


Input ( $S_1$ )	Select ( $S_0$ )	Output (Z)
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

- The logic equation for 4-to-1 multiplexer can be written as

$$Z = \bar{S}_1\bar{S}_0I_0 + \bar{S}_1S_0I_1 + S_1\bar{S}_0I_2 + S_1S_0I_3$$

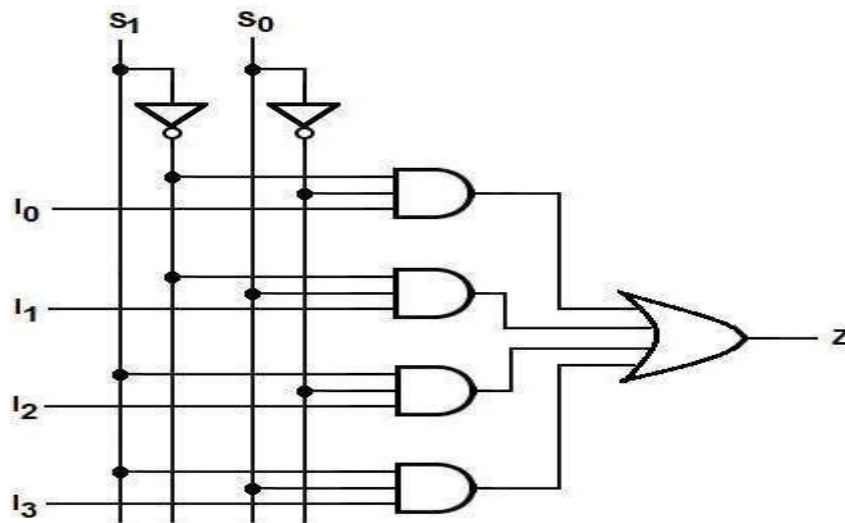**Logic Diagram:****8:1 Multiplexer**

- An 8 to 1 multiplexer has 8 data inputs, 3 select inputs and 1 output. 8 to 1 MUX selects one of eight data inputs using three select inputs

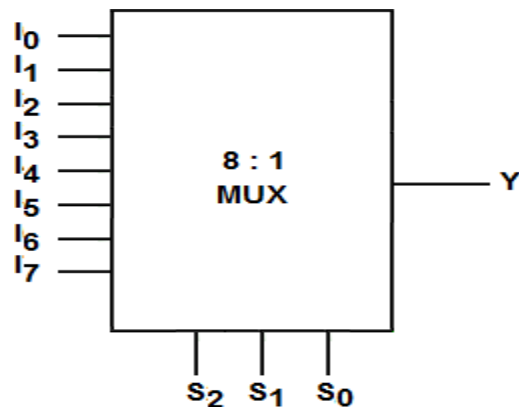**Figure 6.5: 8 to 1 Multiplexer**

- The 8-to-1 MUX acts like an eight-position switch that transmits one of the eight inputs to the output.

**Truth Table:**

elect (S <sub>2</sub> )	Select (S <sub>1</sub> )	Select (S <sub>0</sub> )	Output (Z)
0	0	0	I <sub>0</sub>
0	0	1	I <sub>1</sub>
0	1	0	I <sub>2</sub>
0	1	1	I <sub>3</sub>
1	0	0	I <sub>4</sub>
1	0	1	I <sub>5</sub>
1	1	0	I <sub>6</sub>
1	1	1	I <sub>7</sub>

- The logic equation for the 8 to1 MUX can be written as:

$$Z = \overline{S_2}\overline{S_1}\overline{S_0}I_0 + \overline{S_2}\overline{S_1}S_0I_1 + \overline{S_2}S_1\overline{S_0}I_2 + \overline{S_2}S_1S_0I_3 + S_2\overline{S_1}\overline{S_0}I_4 + S_2\overline{S_1}S_0I_5 + S_2S_1\overline{S_0}I_6 + S_2S_1S_0I_7$$

### **Equipment / components required:**



- Computer with Xilinx - 14.7i. Software Specifications:
- HP Computer i4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Xilinx - 14.7i.

### **Procedure / activity:**


1. Open a Model Sim IDE.
2. Create a new project through the project navigator icon.
3. Add Verilog new source to the project depending on the user requirement.
4. Select the Verilog HDL mode.
5. Assign the inputs and outputs for the system to design.
6. And write the code as given below for the functionality.
7. Synthesize the code and correct the syntax errors if any.
8. Isim Simulator and Behavioral check syntax the Simulation.
9. Observe the output timing waveform and verify it with the truth table.

### **Verilog code:**

2:1 MUX	4:1 MUX	8:1 MUX
<pre> module two_to_one_MUX (I0,I1,S,Y);   input I0;   input I1;   input S;   output Y;    wire S_bar,w1,w2;   not g1(S_bar,S);   and (w1,I0,S_bar);   and (w2,I1,S);   or(Y,w1,w2); endmodule </pre>	<pre> module four_to_one_MUX (I1,I2,I3,I4,S1,S2,Y);   input I1,I2,I3,I4;   input S1,S2;   output Y;    assign Y=((!S1)&amp;(!S2)&amp;I1) ((!S1 )&amp;(S2)&amp;I2) (S1&amp;(!S2)&amp;I3 ) ((S1&amp;S2)&amp;I4); endmodule </pre>	<pre> module eight_to_one_MUX (I1,I2,I3,I4,I5,I6,I7,I8,S1,S2,S3,Y);   input I1,I2,I3,I4,I5,I6,I7,I8;   input S1,S2,S3;   output Y;    assign Y=((!S1)&amp;(!S2)&amp;(!S3)&amp;I1)  ((!S1)&amp;(!S2)&amp;S3&amp;I2) ((!S1)&amp;S2&amp; (!S3)&amp;I3) ((!S1)&amp;S2&amp;S3&amp;I4) (S1 &amp;(!S2)&amp;(!S3)&amp;I5) (S1&amp;(!S2)&amp;S3 &amp;I6) (S1&amp;S2&amp;(!S3)&amp;I7) (S1&amp;S2&amp; S3&amp;I8); endmodule </pre>

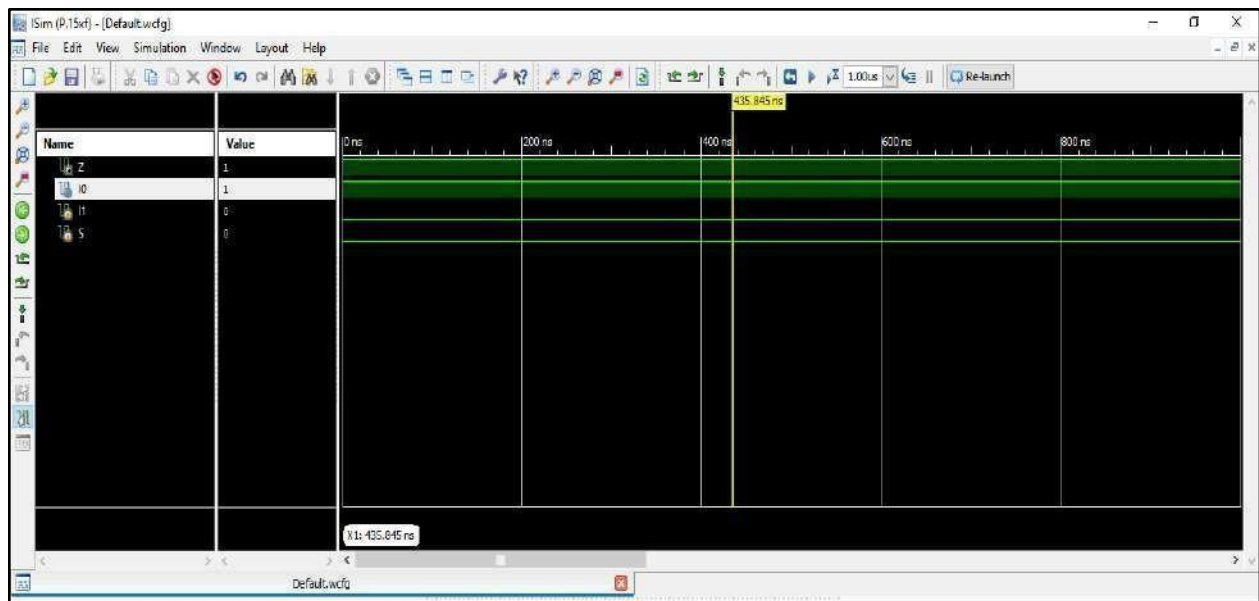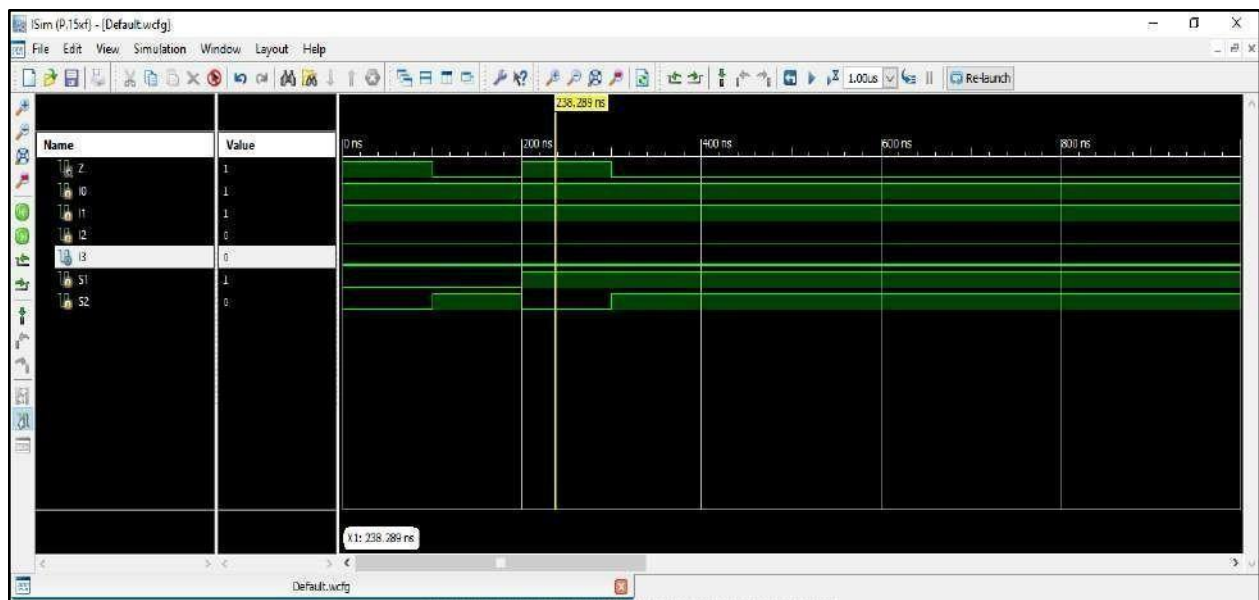**Simulation Output:****2:1 MUX****4:1-MUX**

## 8:1 MUX

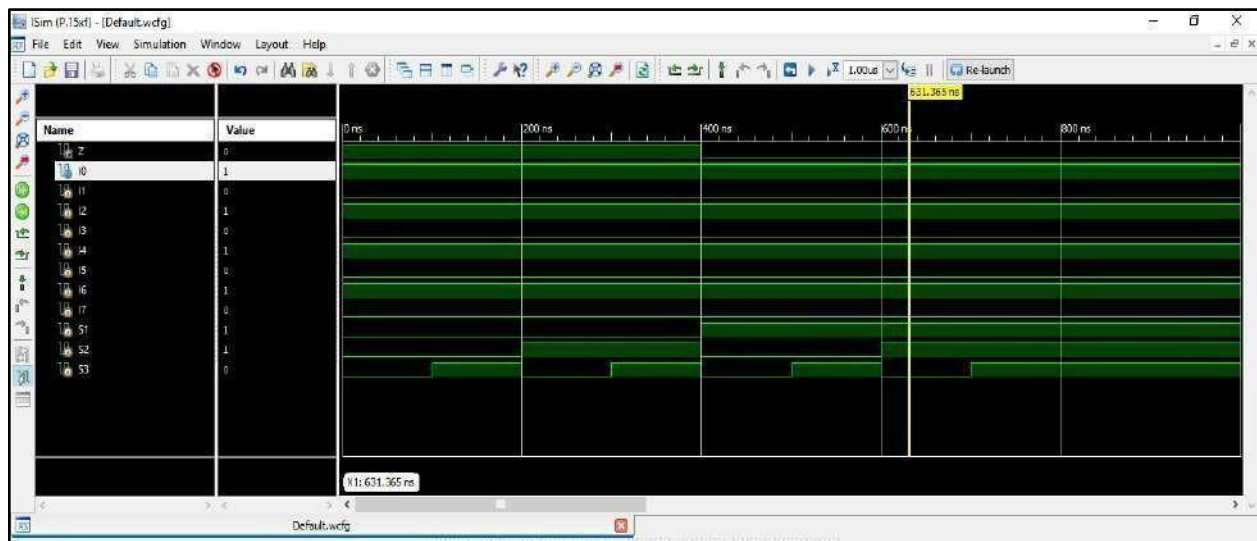**Results & conclusions:**

The Verilog code for Different types of multiplexers like 2:1, 4:1 and 8:1 is simulated and verified.

**Possible viva questions:****1. What is the purpose of a multiplexer?**

**Ans:** A multiplexer is a digital circuit that selects one of several input signals and directs it to a single output.

**2. How does a 2:1 multiplexer differ from a 4:1 multiplexer?**

**Ans:** A 2:1 multiplexer has two inputs, and a 4:1 multiplexer has four inputs.

**3. Explain the role of the select input in a multiplexer.**

**Ans:** A 2:1 multiplexer has two inputs, and a 4:1 multiplexer has four inputs.

**4. What happens when the select input is 0 in a 2:1 multiplexer?**

**Ans:** When the select input is 0 in a 2:1 multiplexer, the output is connected to the first input.

**5. How is the output determined in an 8:1 multiplexer?**

**Ans:** The select input in an 8:1 multiplexer specifies which of the eight inputs is routed to the output.

**6. Can a multiplexer be used to implement logic gates? How?**

**Ans:** Yes, multiplexers can be configured to function as logic gates by appropriately selecting inputs.

**7. Can Verilog code for a 2:1 multiplexer be reused for a 4:1 multiplexer? Why or why not?**

**Ans:** Some code can be reused, but adjustments are needed for the increased number of inputs.

**8. How does the complexity of a multiplexer circuit increase with the number of inputs?**

**Ans:** The complexity of a multiplexer circuit increases linearly with the number of inputs, leading to more logic gates and connections.

**9. Explain the concept of data routing in multiplexers.**

**Ans:** Data routing refers to selecting and transmitting a specific input to the output based on the select input.



**EXPERIMENT NO – 07****Design Verilog program to implement types of De-Multiplexer.****Aim:**

To Design Verilog program to implement Different types of De-multiplexer like 1:2, 1:4 and 1:8.

**Objectives:**

1. Implement Verilog program for 1:2, 1:4, 1:8 Demultiplexer designs.
2. Verify functionality through simulation for accuracy and performance assessment.


**Theory:**

A De-multiplexer is a combinational circuit that has only 1 input line and  $2^N$  output lines. Simply, the multiplexer is a single-input and multi-output combinational circuit. The information is received from the single input lines and directed to the output line. On the basis of the values of the selection lines, the input will be connected to one of these outputs. De-multiplexer is opposite to the multiplexer.

Unlike encoder and decoder, there are  $n$  selection lines and  $2^n$  outputs. So, there is a total of  $2^n$  possible combinations of inputs. De-multiplexer is also treated as **De-mux**.

There are various types of De-multiplexer which are as follows:

**1×2 De-multiplexer:** In the 1 to 2 De-multiplexer, there are only two outputs, i.e.,  $Y_0$ , and  $Y_1$ , 1 selection lines, i.e.,  $S_0$ , and single input, i.e.,  $A$ . Based on the selection value, the input will be connected to one of the outputs. The block diagram and the truth table of the 1×2 multiplexer are given below.

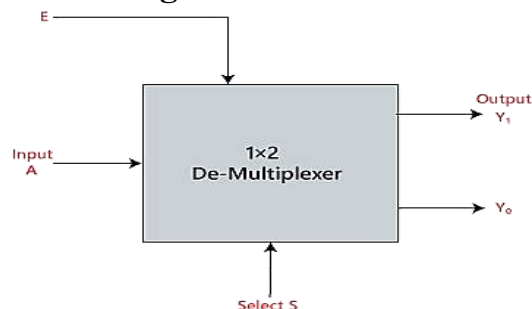**Block Diagram:****Truth Table:**


INPUTS	Output	
$S_0$	$Y_1$	$Y_0$
0	0	A
1	A	0

The logical expression of the term  $Y$  is as follows:

$$Y_0 = S_0' \cdot A$$


$$Y_1 = S_0 \cdot A$$

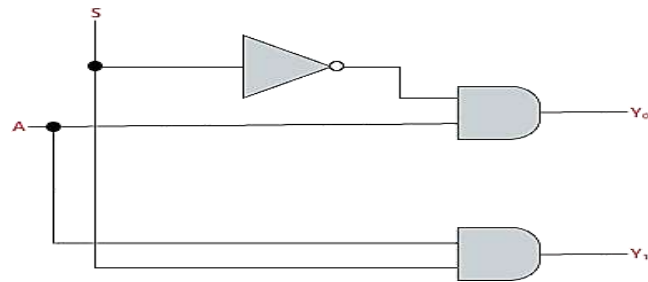Logical circuit of the above expressions is given below:



**1×4 De-multiplexer:** In 1 to 4 De-multiplexer, there are total of four outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$ , 2 selection lines, i.e.,  $S_0$  and  $S_1$  and single input, i.e.,  $A$ . Based on the combination of inputs which are present at the selection lines  $S_0$  and  $S_1$ , the input be connected to one of the outputs. The block diagram and the truth table of the 1×4 multiplexer is given below.

**Block Diagram:**

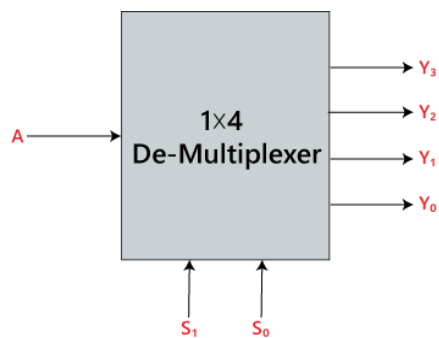

**Truth Table:**

INPUTS		Output			
$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	$A$
0	1	0	0	$A$	0
1	0	0	$A$	0	0
1	1	$A$	0	0	0

The logical expression of the term  $Y$  is as follows:


$$Y_0 = S_1' S_0' A$$

$$Y_1 = S_1' S_0 A$$

$$Y_2 = S_1 S_0' A$$

$$Y_3 = S_1 S_0 A$$

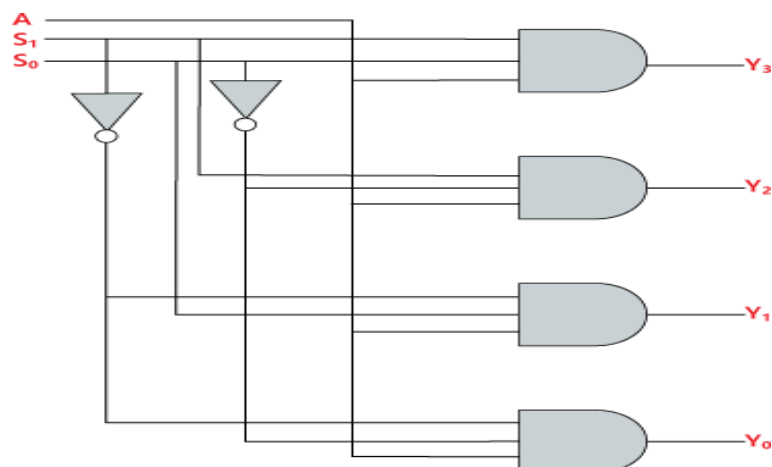
Logical circuit of the above expressions is given below:



**1×8 De-multiplexer:** In 1 to 8 De-multiplexer, there are total of eight outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ ,  $Y_3$ ,  $Y_4$ ,  $Y_5$ ,  $Y_6$ , and  $Y_7$ , 3 selection lines, i.e.,  $S_0$ ,  $S_1$  and  $S_2$  and single input, i.e.,  $A$ . On the basis of the combination of inputs which are present at the selection lines  $S_0$ ,  $S_1$  and  $S_2$ , the input will be connected to one of these outputs. The block diagram and the truth table of the 1×8 de-multiplexer is given below.

**Block Diagram:**

**Truth Table:**

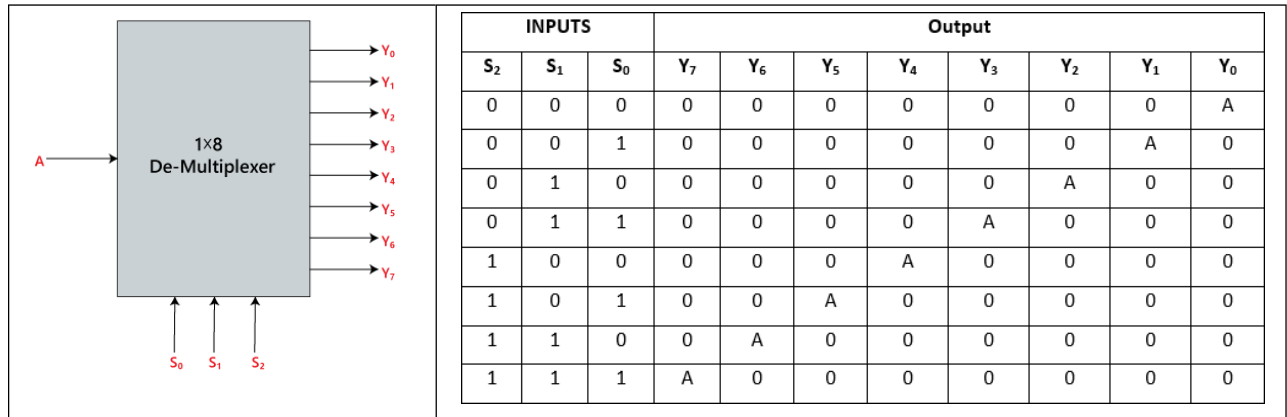

The logical expression of the term  $Y$  is as follows:

$$Y_0 = S_0' \cdot S_1' \cdot S_2' \cdot A$$

$$Y_1 = S_0 \cdot S_1' \cdot S_2' \cdot A$$

$$Y_2 = S_0' \cdot S_1 \cdot S_2' \cdot A$$

$$Y_3 = S_0 \cdot S_1 \cdot S_2' \cdot A$$


$$Y_4 = S_0' \cdot S_1' \cdot S_2 \cdot A$$

$$Y_5 = S_0 \cdot S_1' \cdot S_2 \cdot A$$

$$Y_6 = S_0' \cdot S_1 \cdot S_2 \cdot A$$

$$Y_7 = S_0 \cdot S_1 \cdot S_2 \cdot A$$

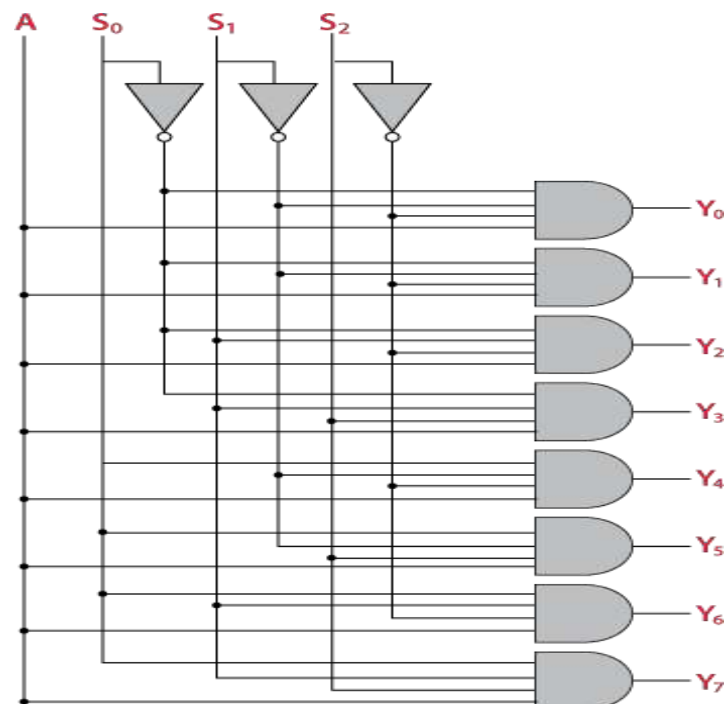Logical circuit of the above expressions is given below:



### **Equipment / components required:**




- Computer with Xilinx - 14.7i.
- HP Computer i4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Software: Xilinx ISE v14.7 IDE

**Procedure / activity:**

1. Open a Model Sim IDE.
2. Create a new project through the project navigator icon.
3. Add Verilog new source to the project depending on the user requirement.
4. Select the Verilog HDL mode.
5. Assign the inputs and outputs for the system to design.
6. And write the code as given below for the functionality.
7. Synthesize the code and correct the syntax errors if any.
8. Isim Simulator and Behavioral check syntax the Simulation.
9. Observe the output timing waveform and verify it with the truth table.

**Verilog code:**

<b>1:2 DEMUX</b>	<b>1:4 DEMUX</b>	<b>1:8 DEMUX</b>
<pre> module demux12_BM(S0,A,Y);   input A, S0;   wire A, S0;   output [1:0] Y;   reg [1:0] Y;   always @(A or S0)   begin     case(S0)       1'b0: Y={A,1'b0};       default: Y={1'b0, A};     endcase   end endmodule </pre>	<pre> module one_four_demux_BM(S,A,Y); input A; wire A; input [1:0] S; wire [1:0] S; output [3:0] Y; reg [3:0] Y;  always @(A or S) begin  case(S) 1'b00: Y= {A,3'b000}; 1'b01: Y= {1'b0, A,2'b00}; 1'b10: Y= {2'b00, A,1'b0}; default: Y= {3'b000, A}; endcase end endmodule </pre>	<pre> module one_eight_demux_BM(S,A,Y); input A; wire A; input [2:0] S; wire [2:0] S; output [7:0] Y; reg [7:0] Y;  always @(A or S) begin  case(S) 0: Y={A,7'b0000000}; 1: Y= {1'b0, A,6'b000000}; 2: Y= {2'b00, A,5'b00000}; 3: Y= {3'b000, A,4'b0000}; 4: Y= {4'b0000, A,3'b000}; 5: Y= {5'b00000, A,2'b00}; 6: Y= {6'b000000, A,1'b0}; default: Y= {7'b0000000, A}; endcase end endmodule </pre>

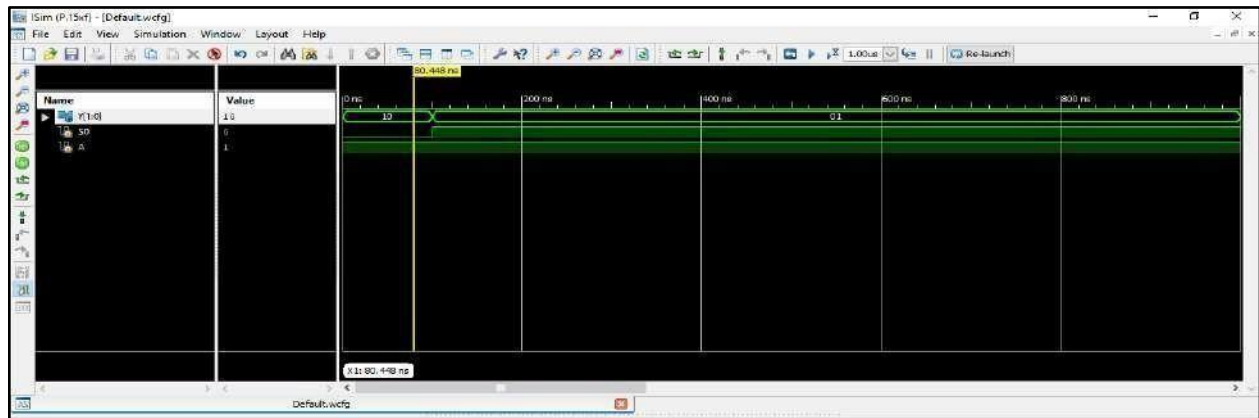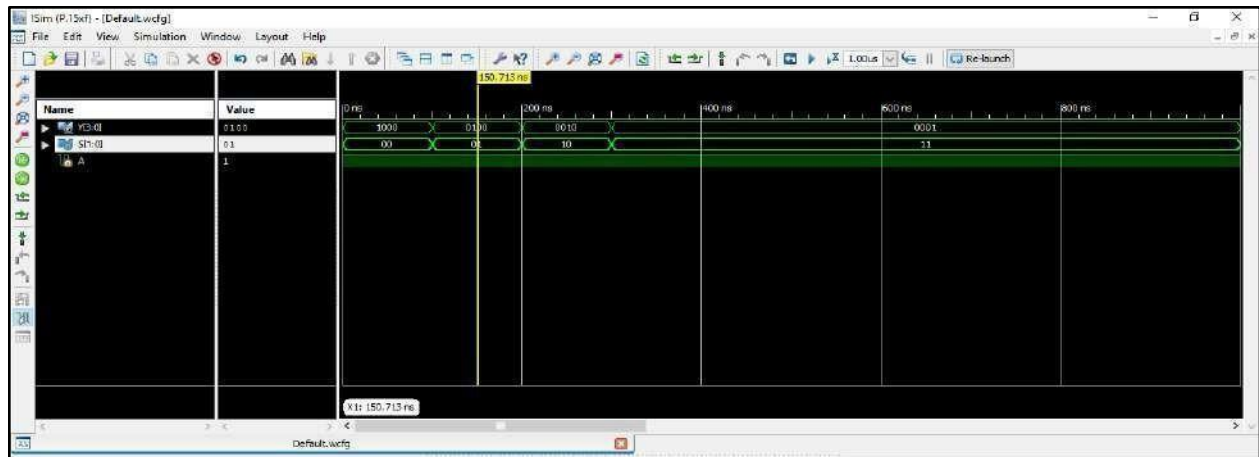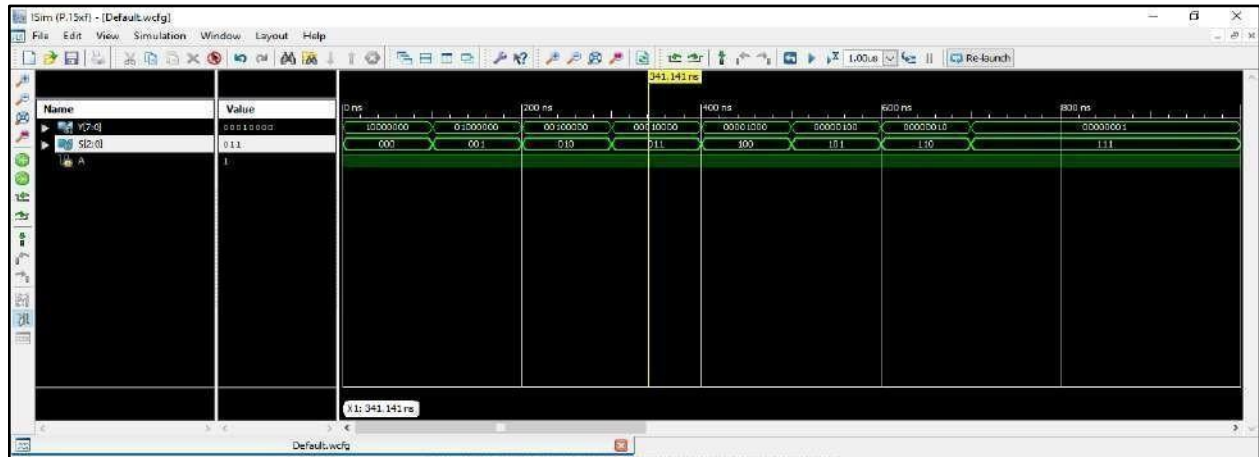**Simulation Output:****1:2 DEMUX****1:4 DEMUX****1:8 DEMUX**

**Results & conclusions:**

The Verilog code for Different types of De-multiplexer like 1:2, 1:4 and 1:8 is simulated and verified.

**Possible viva questions:****1. What is the primary function of a De-Multiplexer (De-Mux)?**

**Ans:** A De-Mux takes a single input and directs it to one of several possible outputs.

**2. Explain the operation of a 1-to-2 De-Multiplexer.**

**Ans:** A 1-to-2 De-Mux selects between two output lines based on the control input.

**3. How does a 1-to-4 De-Multiplexer differ from a 1-to-2 De-Multiplexer?**

**Ans:** A 1-to-4 De-Mux directs one input to one of four outputs based on the control input.

**4. What is the significance of the Enable input in a De-Multiplexer?**

**Ans:** The Enable input allows or inhibits the De-Mux operation, controlling the output based on its state.

**5. Discuss the concept of a Binary De-Multiplexer.**

**Ans:** A Binary De-Mux with  $n$  control lines can select one of  $2^n$  output lines for the input.

**6. How does a De-Multiplexer with multiple outputs, like 1-to-8, function?**

**Ans:** A 1-to-8 De-Mux routes a single input to one of eight possible output lines determined by the control inputs.

**7. What is the purpose of a Priority De-Multiplexer?**

**Ans:** A Priority De-Mux ensures that a specific input is directed to its corresponding output in the presence of multiple inputs.

**8. In what scenarios is a Decoder considered a specialized De-Multiplexer?**

**Ans:** A Decoder acts as a De-Mux by converting a binary code into an equivalent decimal or other code.

**9. How do De-Multiplexers contribute to data routing in communication systems?**

**Ans:** De-Muxes route data to specific channels, aiding in the distribution of information in communication networks.

**10. Explain how De-Multiplexers enhance flexibility in digital circuits.**

**Ans:** De-Muxes provide flexibility by enabling the selection of different output lines for a single input based on control signals.

**EXPERIMENT NO – 08****Design Verilog program for implementing various types of Flip-Flops such as SR, JK and D**

**Aim:** To design and simulate Verilog modules for three different types of flip-flops (SR, JK, and D) using behavioral modeling. The program should demonstrate the functionality and behavior of these flip-flops under various input conditions.



**Objectives:**

- Implement Verilog modules for SR, JK, and D flip-flops using behavioral modeling. Develop a testbench to simulate the behavior of the implemented flip-flops.
- Apply different input conditions to the flip-flops in the testbench to observe their responses.
- Verify that the flip-flops exhibit the expected sequential logic behavior, such as state changes and toggling.


**Theory:**

Flip-flops are synchronous bitable devices. The term synchronous means the output changes state only when the clock input is triggered. That is, changes in the output occur in synchronization with the clock. A flip-flop circuit has two outputs, one for the normal value and one for the complement value of the stored bit. Since memory elements in sequential circuits are usually flip-flops, it is worth summarizing the behavior of various flip-flop types before proceeding further. Flip-flops can be divided into four basic types: SR, JK, D and T. They differ in the number of inputs and in the response invoked by different value of input signals. The four types of flip-flops are defined in the Table 8.1. Each of these flip-flops can be uniquely described by its graphical symbol, its characteristic table, its characteristic equation or excitation table. All flip-flops have output signals Q and Q'.

**Table 8.1: Flip-flops and their properties**

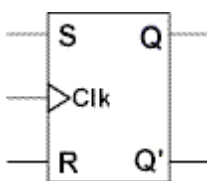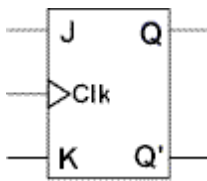Flip-Flop Name	Flip-Flop Symbol	Characteristic Table	Characteristic Equation	Excitation Table																																			
SR		<table><tr><th>S</th><th>R</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>?</td></tr></table>	S	R	Q(next)	0	0	Q	0	1	0	1	0	1	1	1	?	$Q(\text{next}) = S + R'Q$ $SR = 0$	<table><tr><th>Q</th><th>Q(next)</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table>	Q	Q(next)	S	R	0	0	0	X	0	1	1	0	1	0	0	1	1	1	X	0
S	R	Q(next)																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	?																																					
Q	Q(next)	S	R																																				
0	0	0	X																																				
0	1	1	0																																				
1	0	0	1																																				
1	1	X	0																																				
JK		<table><tr><th>J</th><th>K</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>Q'</td></tr></table>	J	K	Q(next)	0	0	Q	0	1	0	1	0	1	1	1	Q'	$Q(\text{next}) = JQ' + K'Q$	<table><tr><th>Q</th><th>Q(next)</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>X</td></tr><tr><td>1</td><td>0</td><td>X</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table>	Q	Q(next)	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0
J	K	Q(next)																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	Q'																																					
Q	Q(next)	J	K																																				
0	0	0	X																																				
0	1	1	X																																				
1	0	X	1																																				
1	1	X	0																																				

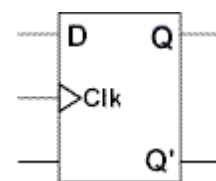

D		<table><tr><th>D</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q(next)	0	0	1	1	$Q(\text{next}) = D$	<table><tr><th>Q</th><th>Q(next)</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Q	Q(next)	D	0	0	0	0	1	1	1	0	0	1	1	1
		D	Q(next)																						
		0	0																						
		1	1																						
		Q	Q(next)	D																					
0	0	0																							
0	1	1																							
1	0	0																							
1	1	1																							

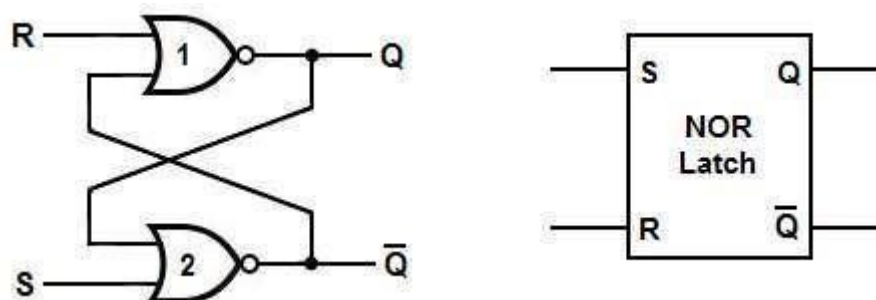
**Logic diagram**

Figure 8.1: SR (a) NOR Gate latch (b) Symbol

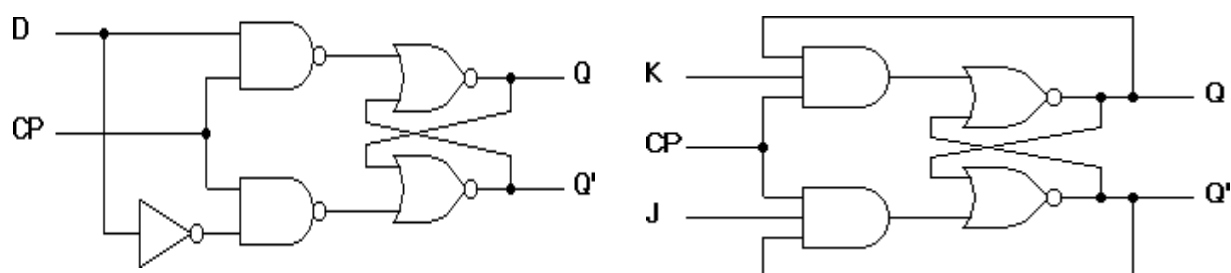


Figure 8.2: D- Flip Flop

Figure 8.3: JK Flip Flop

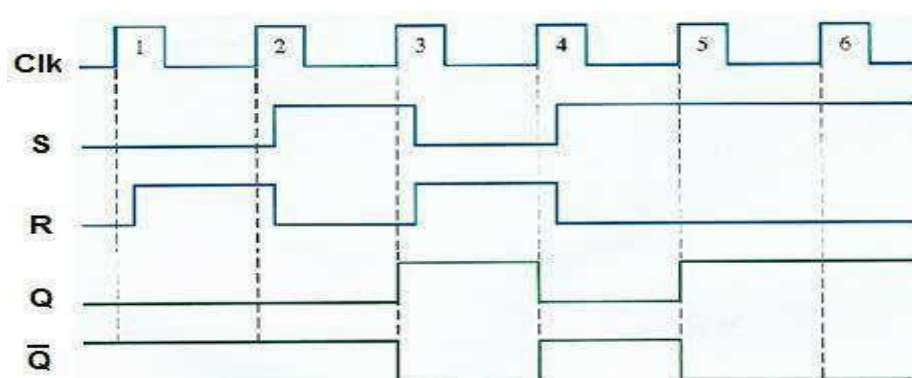
**Graphs**

Figure 8.4: Timing diagram of SR Flip-Flop

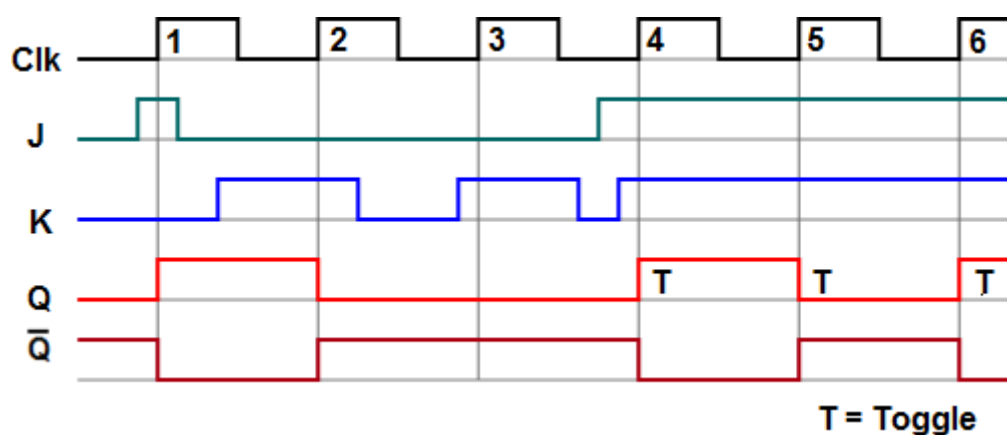


Figure 8.5: Timing diagram of JK Flip-Flop

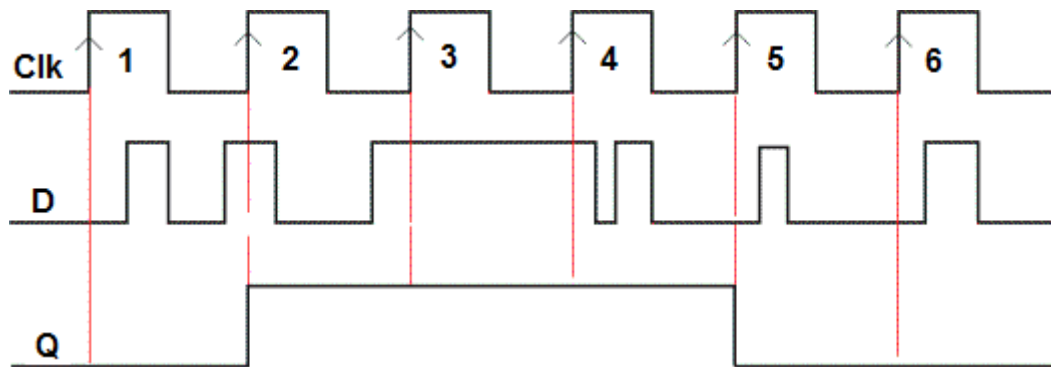


Figure 8.6: Timing diagram of D Flip-Flop

**Equipment / components required:**

- Computer with Modelsim Software Specifications:
- HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk
- Softwares: Modelsim - 5.7c, Xilinx - 14.1i.

**Procedure:**

1. Open a Model Sim IDE.
2. Create a new project through the project navigator icon.
3. Add Verilog new source to the project depending on the user requirement.
4. Select the Verilog HDL mode.
5. Assign the inputs and outputs for the system to design.
6. And write the code as given below for the functionality.
7. Synthesize the code and correct the syntax errors if any.
8. Isim Simulator and Behavioral check syntax the Simulation.
9. Observe the output timing waveform and verify it with the truth table.


**Verilog code:**

1. SR Flip-Flop	2. JK Flip Flop	3. D Flip Flop
<pre> module srlax(   input wire S,   input wire R,   input output reg Q,   output wire Q_bar ); always @(S,R) begin   if (S &amp;&amp; ~R)     Q &lt;= 1'b1;   else if (~S &amp;&amp; R)     Q &lt;= 1'b0;   else if (S==0 &amp;&amp; R==0)     Q &lt;= Q;   else if (S==1 &amp;&amp; R==1)     Q &lt;= 1'bz;   end   assign Q_bar = ~Q; endmodule </pre>	<pre> module JK_FF(   input wire j,   input wire k,   output reg Q,   output wire Q_bar );  always @(j, k) begin   if (j &amp;&amp; ~k)     Q &lt;= 1'b1;   else if (~j &amp;&amp; k)     Q &lt;= 1'b0;   else if (j==0 &amp;&amp; k==0)     Q &lt;= Q;   else if (j==1 &amp;&amp; k==1)     Q &lt;= !Q;   end   assign Q_bar = ~Q; endmodule </pre>	<pre> module D_FF(   input wire D,   output reg Q,   output wire Q_bar );  always @(D) begin   if (D==0)     Q &lt;= 0;   else     Q &lt;= 1; end  assign Q_bar = ~Q; endmodule </pre>


	endmodule	
--	-----------	--

## Simulation Output:


### 1. SR Flip-Flop

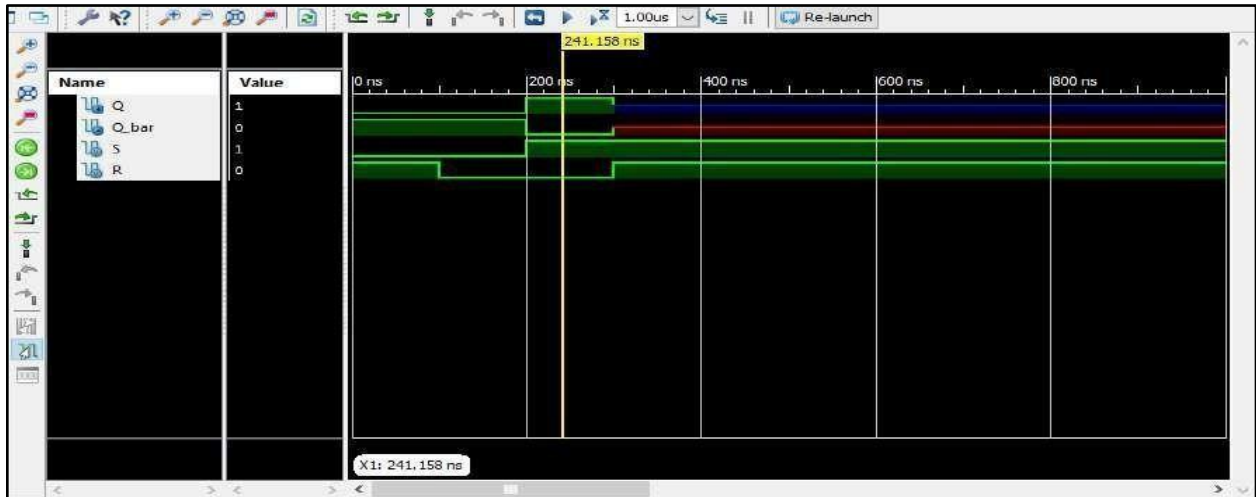

### 2. JK Flip Flop

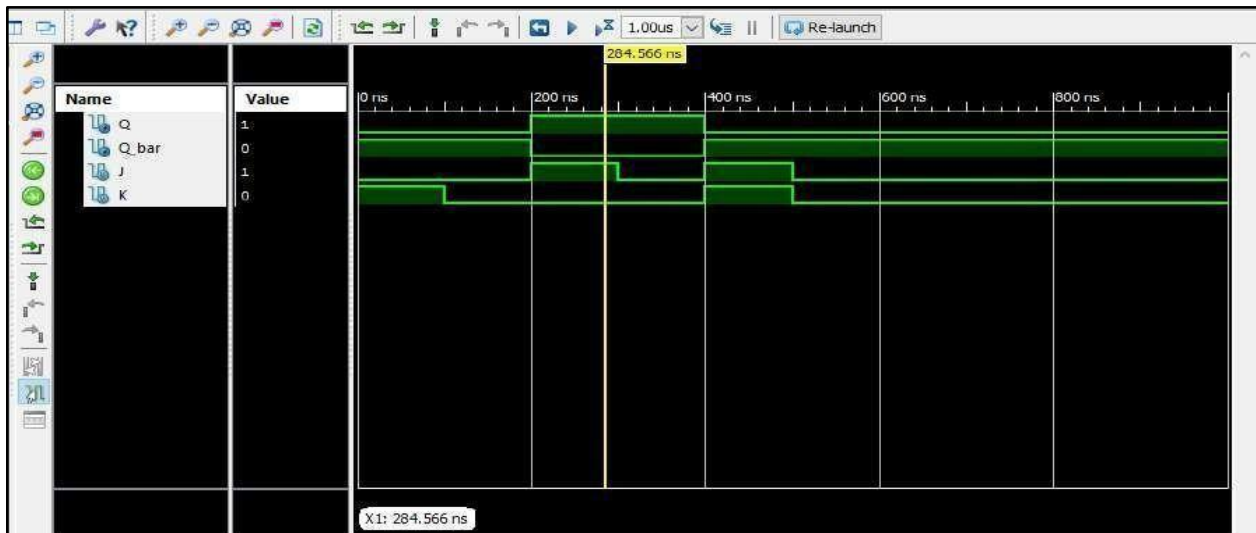

### 3. D Flip Flop

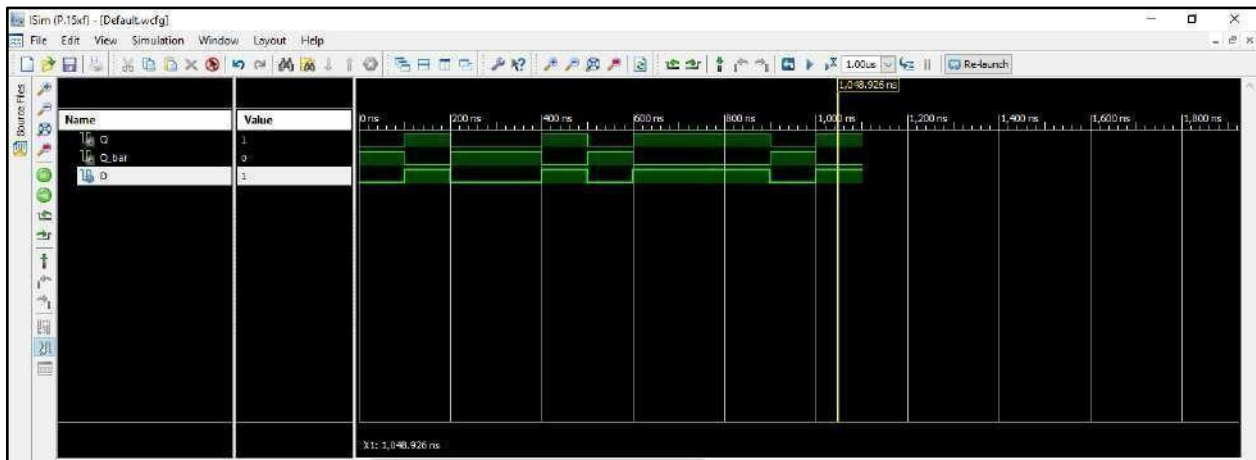

#### Results & conclusions:

The Verilog code for Different types various types of Flip-Flops such as SR, JK and D is simulated and verified

#### Possible viva questions:

- What is an SR flip-flop, and what are its primary characteristics?**  
An SR flip-flop is a digital circuit with Set (S) and Reset (R) inputs, storing binary information.
- What are the possible states of an SR flip-flop?**  
Possible SR flip-flop states: Set ( $Q=1$ ), Reset ( $Q=0$ ), Hold ( $Q$  unchanged).
- How does the presence of an illegal state in an SR flip-flop affect its operation?**  
Illegal states in SR flip-flop may lead to undefined behavior or undesired output transitions.
- Describe a real-world application where an SR flip-flop is useful.**  
SR flip-flops are used in memory circuits, latch circuits, and control systems for state storage.
- How can you use an SR flip-flop to create a simple toggle circuit?**  
Connect S and R inputs of an SR flip-flop, toggling between Set and Reset states.
- Explain the concept of setup time and hold time in the context of an SR flip-flop.**  
Setup time ensures stable inputs before a clock edge, while hold time maintains stability after the edge.
- What are the features that distinguish a JK flip-flop from an SR flip-flop?**  
JK flip-flop features include a toggle functionality, preventing illegal states, and a versatile behavior distinguishing it from an SR flip-flop.
- How is a JK flip-flop used to create a toggle circuit?**  
Connecting J and K inputs allows a JK flip-flop to function as a toggle circuit, changing state on each clock edge.
- In what applications is a JK flip-flop preferred over other types of flip-flops?**  
JK flip-flops are preferred in applications requiring toggling behavior, memory storage, and sequential logic due to their versatility and prevention of illegal states.
- In what applications is a D flip-flop typically used for data storage and transfer?**  
D flip-flops are used in applications like registers, memory units, and sequential logic circuits for reliable data storage and transfer.